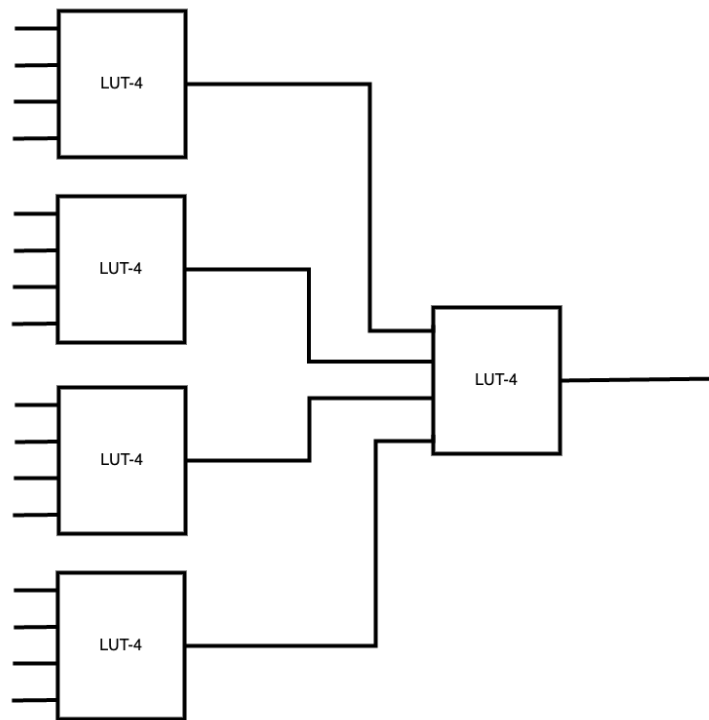


# EECS 151/251A Discussion 3

February 2, 2024

## Problem 1: LUTs and Functions

Lookup Tables (LUTs) are the fundamental building blocks of FPGA architectures. A LUT- $N$  can implement **any**  $N$  input logic function (ex. a LUT-4 can implement any logic function with four logical inputs). On an FPGA, LUTs can be connected together through special routing to implement functions with even more inputs. Consider the following arrangement of five LUT-4 blocks:



How many logic functions can this chain of LUT-4's implement?

**Solution:**


Let's break it down. **A function is a logical expression.** How many functions can single bit implement? 4. Bit A can be either 0 or 1, and can map to 0 or 1.

1.  $A \rightarrow 0$
2.  $A \rightarrow 1$
3.  $\bar{A} \rightarrow 0$
4.  $\bar{A} \rightarrow 1$

From this we can establish a general rule:  $2^{2^n}$  for a LUT-N. Therefore, each LUT-4 can implement  $2^{2^4} = 2^{16} = 65536$  functions. Since the inputs to the last LUT-4 is another LUT-4, each bit represents  $2^{2^4}$  functions. Therefore, the total number of functions is  $(2^{16})^5$ .

Challenge yourself.

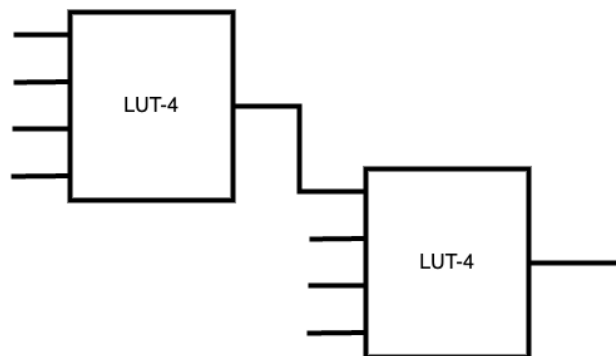
1. How many functions can be produced if the last LUT-4 is removed and the outputs are concatenate?  $(2^{16})^4$
2. How many functions can be produced for the following circuit:



The answer is  $2^{2^{32}}$ .
 
## Problem 2: Self Starting Ring Counter

A ring counter is a special counter composed of flip-flops daisy-chained together to form a shift register and the output of the last flip-flop is connected to the output of the first. Below is a variant of self starting ring counter. (**Note:** the last flip-flops output is not the input to the first, but it's close enough to call it a ring counter :-)). It is self starting because there is no reset. The counter will reset itself! The counter is read out such that the first register is the LSb of the count value.



1. How does this self-initialize itself?
2. What type of counter is this?
3. Assume the register are initialized as 0, 1, 0, 1, 0. Create a table showing clock cycle, input to the chain, value of each register. Provide a waveform diagram for the first 10 cycles after initialization.
4. How does the circuit behave in steady state (steady state means after hundreds of cycle)?
5. This behavior can be create using a regular incrementing counter and a decoder. Write Verilog for this implementation.

### Solution:

The NOR gate takes as input all *except* the last flip-flop in the shift register. Therefore, the NOR output is 1 only if all of the first four registers are zero. Since, the NOR output is the input of the shift register, wherever the previous condition occurs the shift register is initialize with a 1. Note this occurs regardless of the value in the last flip-flop.

1. The input to the shift register is 1 when the first four flip-flops are zero.
2. A one-hot counter
- 3.


Cycle	NOR Output	Reg0	Reg1	Reg2	Reg3	Reg4
0	0	1	1	0	1	0
1	0	0	1	1	0	1
2	0	0	0	1	1	0
3	0	0	0	0	1	1
4	1	0	0	0	0	1
5	0	1	0	0	0	0
6	0	0	1	0	0	0
7	0	0	0	1	0	0
8	0	0	0	0	1	0
9	1	0	0	0	0	1
10	0	1	0	0	0	0

4. It counts in powers of two: 1, 2, 4, 8, 16, 1, 2, 4, ...

```
5. module ring_cnt(  
    input clk,  
    output reg [4:0] cnt);  
  
    integer j; // Used for bit reversal  
  
    wire [4:0] reg_in; // Input to register  
    reg [5:0] reg_out; // Output of register  
  
    // Create shift register  
    genvar i;  
    generate  
        for (i=0; i<5; i=i+1) begin  
            REGISTER regX ( .clk(clk),  
                            .d([reg_in]),  
                            .q(reg_out[i]));  
        end  
    endgenerate  
  
    // Procedural Assignment  
    always @(*) begin  
        for (j=0; j<5; j=j+1) begin  
            cnt[j] = reg_out[4-j];  
        end  
    end  
  
    // Signal Assignment  
    assign reg_in = {reg_out[3:0], ~|reg_out[3:0]};  
  
endmodule
```


### Problem 3: Decoder-Based Multiplexer

 - (a) Design a 4-to-1 multiplexer using one of the decoders you designed above. The select signals must be input to the decoder and must not be used anywhere else. Provide an exhaustive test.
- (b) What could be a potential benefit of using this decoder-based multiplexer against the following design:



#### Solution:

- (a) Diagram:

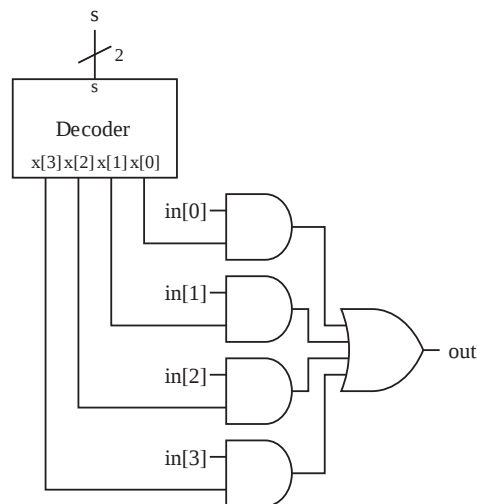

Design:

```
`include "decoder.v"

module multiplexer(
    input [1:0] s,
    input [3:0] in,
    output      out
);

    wire [3:0] x;
    wire      t0, t1, t2, t3;

    decoder1 dc1(.s(s), .x(x));

    and(t0, in[0], x[0]);
    and(t1, in[1], x[1]);
    and(t2, in[2], x[2]);
    and(t3, in[3], x[3]);
    or(out, t0, t1, t2, t3);

endmodule
```

Testbench:

```

module multiplexer_tb;
  reg [1:0] s;
  reg [3:0] in;
  reg      expected;
  wire    out;

  // loop variables
  integer i, j;

  // instantiate duts
  multiplexer mux1(.s(s), .in(in), .out(out));

  // expected outputs
  always @(*) begin
    case (s)
      2'b00:  expected = in[0];
      2'b01:  expected = in[1];
      2'b10:  expected = in[2];
      2'b11:  expected = in[3];
      default: expected = 1'bx;
    endcase
  end

  // begin test
  initial begin
    $dumpfile("dump.vcd");
    $dumpvars;
    for(j = 0; j < 16; j = j + 1) begin
      in = j;
      for(i = 0; i < 4; i = i + 1) begin
        s = i;
        #1;
        $display("s: %b, in: %b, out: %b, expected: %b",
                s, in, out, expected);
        // Break early if failed
        if(out !== expected) begin
          $display("FAILED, expected %b, got %b",
                  expected, out);
          $finish();
        end
      end
    end
    $display("ALL TESTS PASSED!");
    $finish();
  end

```

**endmodule**

- (b) Smaller delay (fewer logic levels) from data input to output, trading off delay from select signals to output.