

EECS 151/251A

Spring 2024


Digital Design and Integrated Circuits

Instructors:
Wawrzynek

Lecture 10: CMOS2

Announcements

 
- ❑ Monday is an Academic Holiday
- ❑ New Midterm Date/Time:
 - ❑ **Tue Mar 12 2024 7:00-10:00PM**
 - ❑ **MOFF101, VLSB2040**
- ❑ Lecture Schedule change:
 - ❑ Monday Mar 11, in-class MT review



CMOS Transistors

Transistor Strength and Symmetry

 1. Transistor “strength” proportional to W/L . In digital circuits, L is almost always minimal allowed by process.




2. MOS transistors are symmetrical devices (Source and drain are interchangeable). But usually designed to be used in one direction.


For nFET, source is the node w/ the lowest voltage. For pFET source is node with highest voltage.

Circuit Layout Examples

□ 2-input NAND

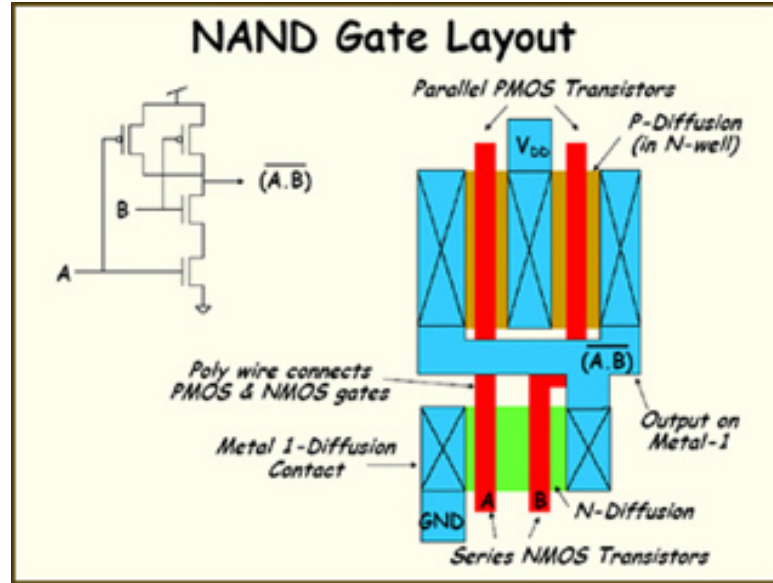


 NAND gate layout from Lecture 3: CMOS Technology and Logic Gates. (Image by Professors Arvind and Asanovic.)




from Ji Li

MOS Transistor as a Resistive Switch

 


*Let's look beneath the abstraction:
 V_T and R_{on}*

MOSFET Threshold Voltage


 


 Transistor "turns on" when V_{gs} is $> V_t$.




Transistor “resistance”

- Nonlinear I/V characteristic:

 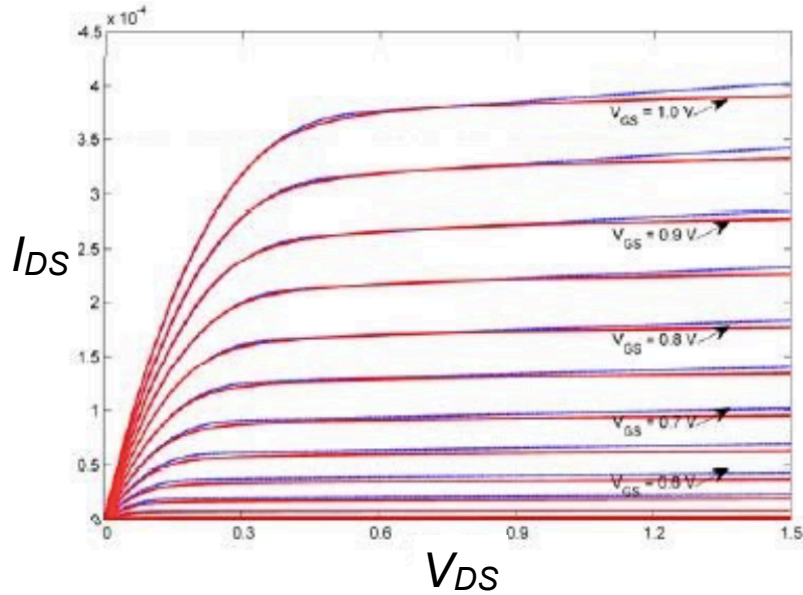


- But, linearizing makes all delay and power calculations simple (usually just 1st order ODEs):

ON/OFF Switch Model of MOS Transistor

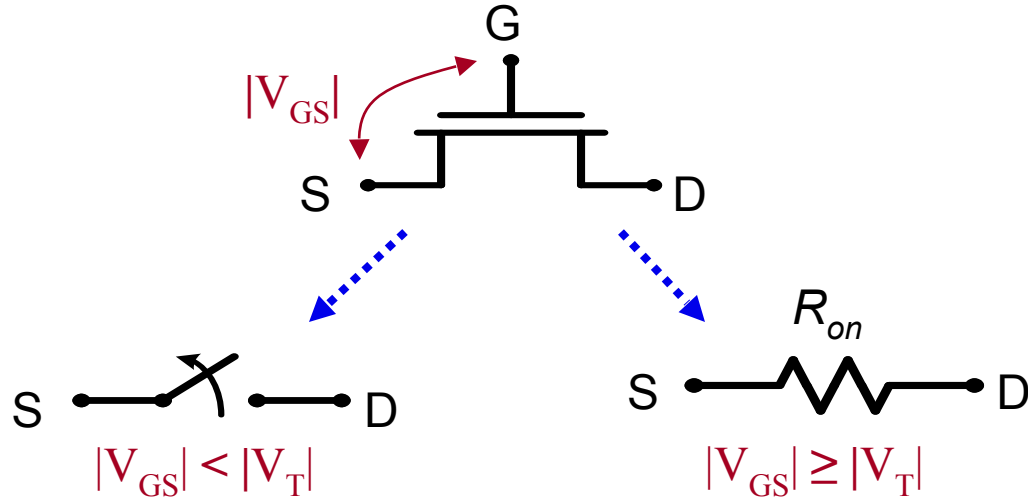

 Plot on a "Log" Scale to See "Off" Current




$$V_{ds} = V_{dd}$$



Process engineers can:

increase I_{on} by lowering V_t - but that raises I_{off}
decrease I_{off} by raising V_t - but that lowers I_{on} .

$I_{off} \approx 10 \text{ nA}$

 


Latest Modern Process

  


Transistor channel is a raised fin.

 
Gate controls channel from sides and top.




A More Realistic Switch

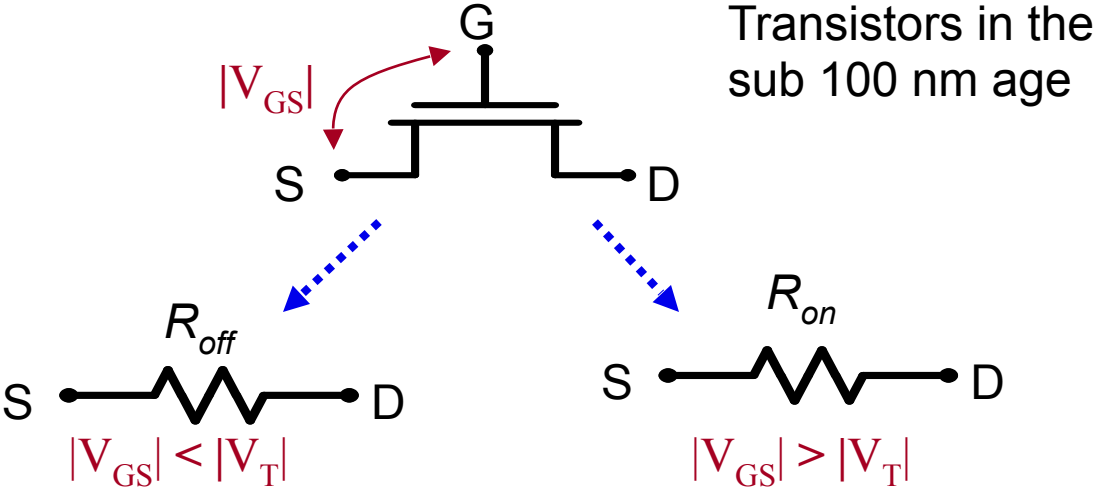

A Logic Perspective

 


A Complementary Switch

 

$Y=Z$ if $X=0$


PMOS Transistor

 

$V_{GS} < 0$
 $|V_{GS}| > |V_T|$

Remember, source is the node w/ the highest voltage.



The CMOS Inverter: A First Glance

 

Represents the sum of all the capacitance at the output of the inverter and everything to which it connects: (drains, interconnections gate capacitance of next gate(s))


The Switch Inverter

First-Order DC Analysis*

  

$$V_{OL} = 0$$
$$V_{OH} = V_{DD}$$

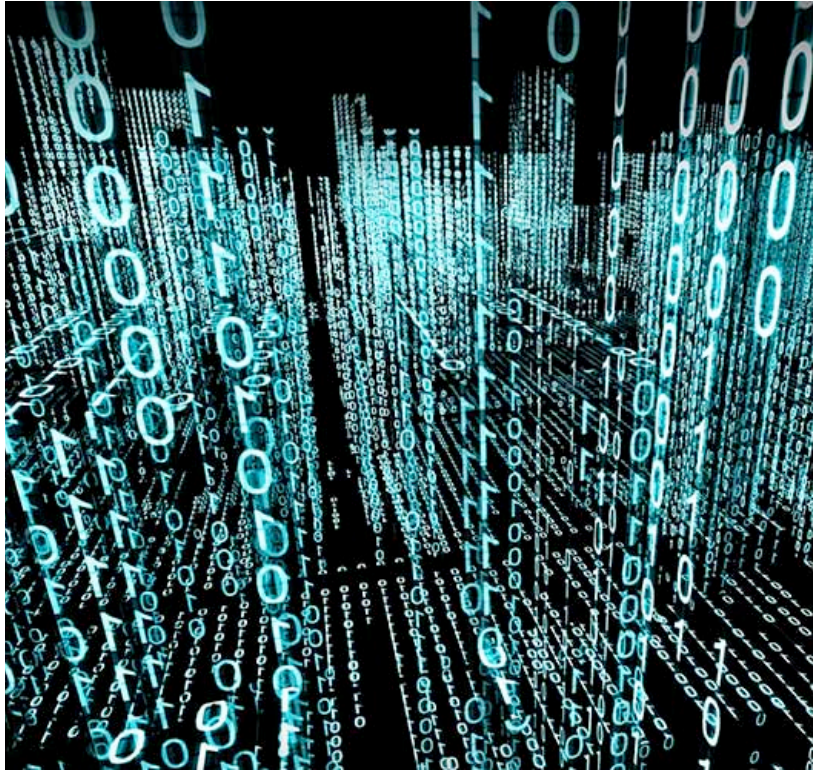*First-order means we will ignore Capacitance.




Switch logic

Static Logic Gates (most common and straight forward type of gate)


- At every point in time (except during the switching transients) each gate output is connected to either V_{DD} or V_{GND} via a low resistive path.
- The output of the gate assumes at all times the value of the Boolean function implemented by the circuit (ignoring, once again, the transient effects during switching periods).

Example: CMOS Inverter

 

Building logic from switches (NMOS)


Series

 

AND

$Y = X$ if *A* AND *B*

Parallel

 


OR

$Y = X$ if *A* OR *B*

(output undefined if condition not true)

Logic using inverting switches (PMOS)


Series

 

NOR

$$Y = X \text{ if } \bar{A} \text{ AND } \bar{B} \\ = \overline{A + B}$$

Parallel

 

NAND


$$Y = X \text{ if } \bar{A} \text{ OR } \bar{B} \\ = \overline{AB}$$

(output undefined if condition not true)

Example Gate: NAND


A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

- pull-down network: $G = AB \Rightarrow$ Conduction to GND
- pull-up network: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

Static Complementary CMOS

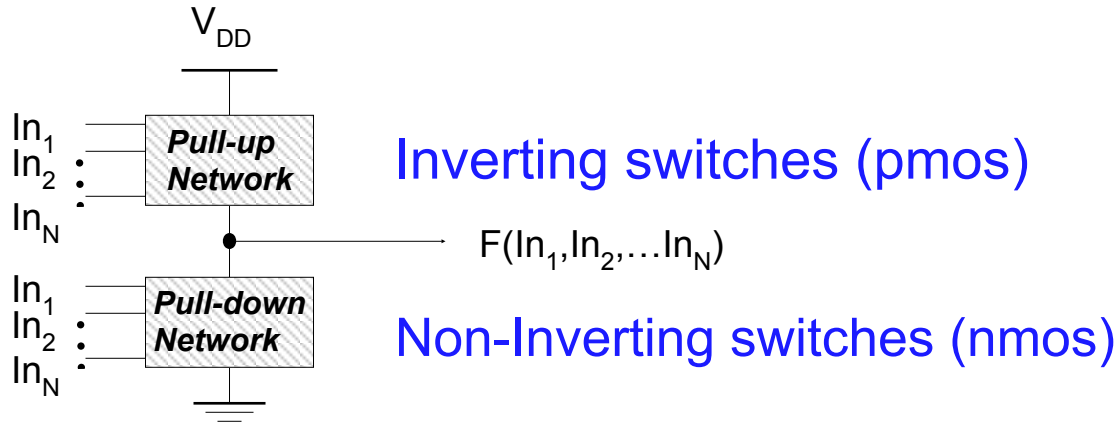

PUN and PDN are dual logic networks:

series connections in the PUN are parallel connections in the PDN
parallel connections in the PUN are series connections in the PDN


PUN and PDN functions are complements:

guarantees they are mutually exclusive, under all input values,
one or the other is conductive, but never both!

Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 


Complex CMOS Gate

$$\overline{\text{OUT}} = \overline{D + A \cdot (B + C)}$$

 
$$\text{OUT} = \overline{D \cdot A + B \cdot C}$$



Graph Models for Duals

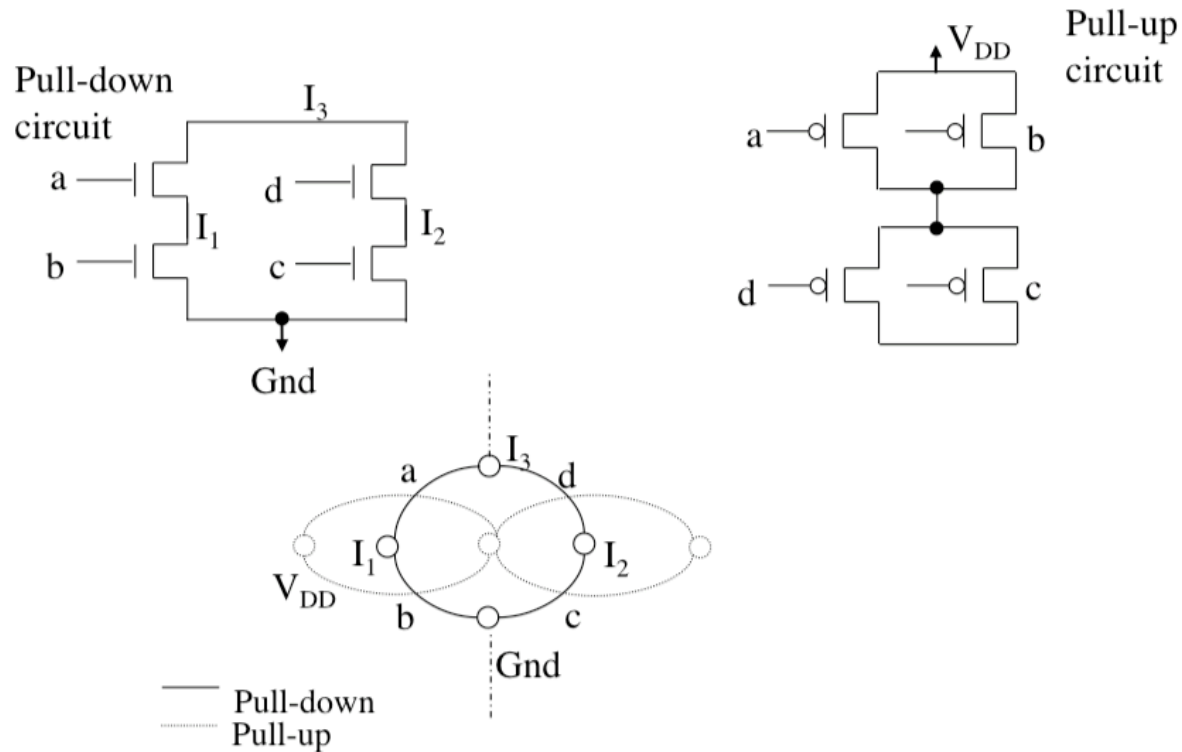

Non-inverting logic

 





Non-Inverting switches (nmos)

Inverting switches (pmos)

Why is this a bad idea?


PUN and PDN are **dual** logic networks
PUN and PDN functions are **complementary**

Switch Limitations

  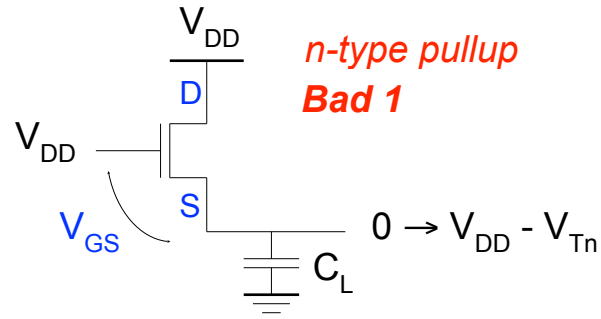 

Tough luck ...


“Static” CMOS gates

 


Inverting switches (PMOS transistors)

Non-Inverting switches (NMOS transistors)

- Static CMOS gates are always inverting

 


AND = NAND , INV

 

Transmission Gate

 - ❑ Transmission gates are the way to build ideal “switches” in CMOS.
- ❑ In general, for an ideal switch, both transistor types are needed:
 - ❑ nFET to pass zeros.
 - ❑ pFET to pass ones.
- ❑ The transmission gate is bi-directional (unlike logic gates).




if en==1 then A connects to B

- ❑ Does not directly connect to Vdd and GND, but can be combined with logic gates or inverters to simplify many logic functions.



Transmission-gate Multiplexor

2-to-1 multiplexor:

$$c = sa + s'b$$

 

Switches simplify the implementation:

  


Compare the cost to logic gate implementation.

Care must be taken to not string together many pass-transistor stages.
Occasionally, need to “rebuffer” with static gate.

4-to-1 Transmission-gate Mux

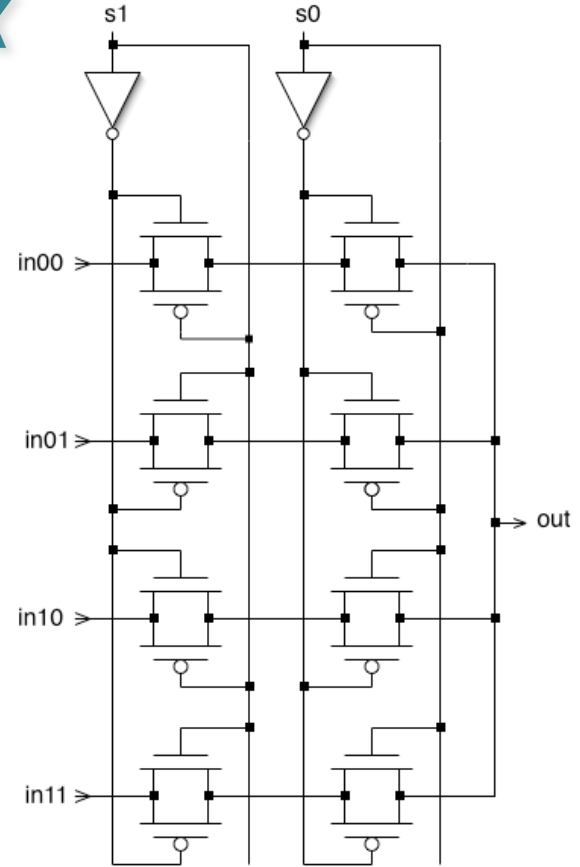
- ❑ The series connection of pass-transistors in each branch effectively forms the AND of $s1$ and $s0$ (or their complement).
- ❑ Compare cost to logic gate implementation



Any alternate solutions?

Alternative 4-to-1 Multiplexor

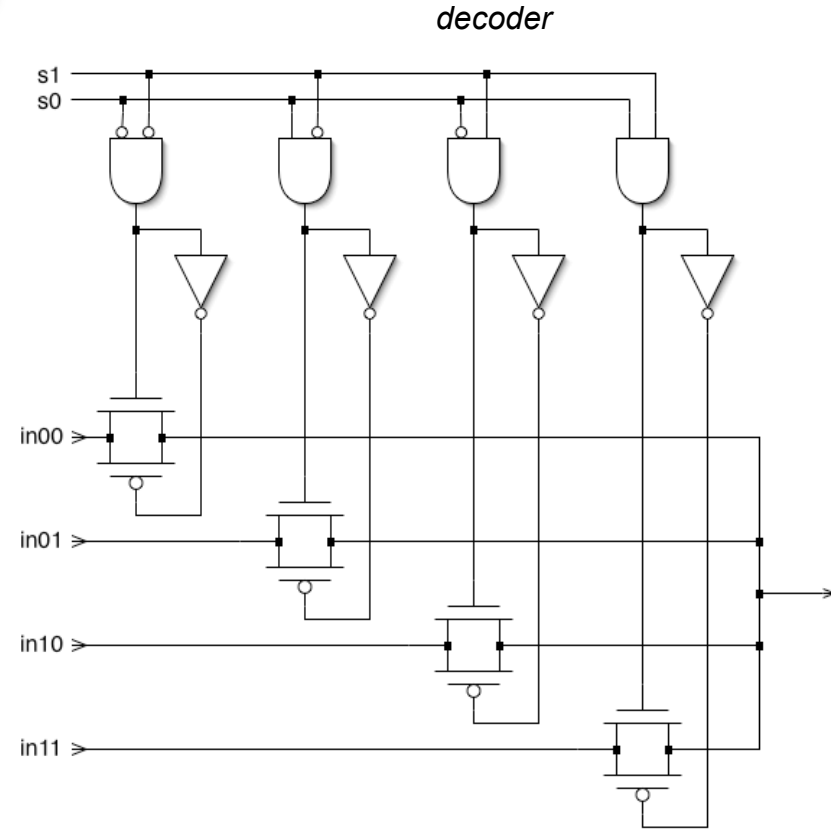
- ❑ This version has less delay from in to out.
- ❑ In both versions, care must be taken to avoid turning on multiple paths simultaneously (shorting together the inputs).




Tri-state Buffers

Tri-state Buffer:



OE	IN	OUT
0	0	Z
0	1	Z
1	0	0
1	1	1

 

“high impedance” (output disconnected)

 


CMOS Implementation

  


transmission gate provide the isolation: usually designed this way

Variations:

 

OE	IN	OUT
0	-	Z
1	0	1
1	1	0


Inverting buffer

 

OE	IN	OUT
0	0	0
0	1	1
1	-	Z


Inverted enable

Tri-state Buffers

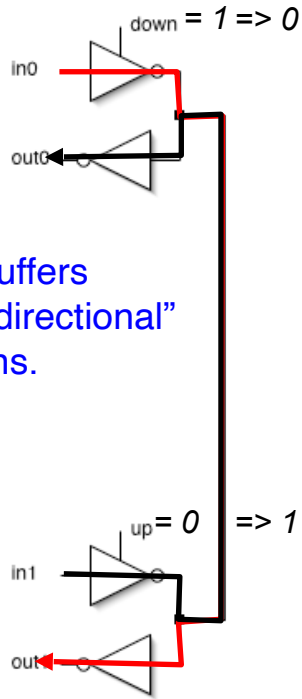


Tri-state buffers enable “bidirectional” connections.

 Tri-state buffers are used when multiple circuits all connect to a common node or wire. Only one circuit at a time is allowed to drive the bus. All others “disconnect” their outputs, but can “listen”.





Tri-state Based Multiplexor



Multiplexor:

 

If $s=1$ then $c=a$ else $c=b$

 
 


  Transistor Circuit for inverting-multiplexor:




Latches and Flip-flops

Positive Level-sensitive *latch*:

  


Latch Implementation:

 


When the clock is high, the latch is “transparent”, when clock is low, it holds the last seen value


Positive edge-triggered flip-flop

 

 A flip-flop “samples” on the positive clock-edge, and then “holds” value.




Sensing: When clock is low

 


A flip-flop “samples” on the positive clock-edge, and then “holds” value.


Sampling latch

 


Holding latch

 

$clk = 0$
 $clk' = 1$

 


Ready to capture new value on clock edge

 


Is outputting last previous captured value.

Capture: When clock goes high

 


A flip-flop “samples” on the positive clock-edge, and then “holds” value.


Sampling latch

 

Holding latch

 


$clk = 1$
 $clk' = 0$

 

Remembers value just captured.


Outputs value just captured.

Return to sensing: When clock is low

 


A flip-flop “samples” just before the edge, and then “holds” value.


Sampling latch

 


Holding latch

 

$clk = 0$
 $clk' = 1$

 


Ready to capture new value on clock edge

 

Continue to output captured value.

Tri-state-Inverter Latch implementation

 - ❑ Commonly used in standard cell flip-flops.
- ❑ More transistors than pass-transistor version, but more robust.
- ❑ Lays out well with modern layout rules.



Negative Level-sensitive latch: