

EECS 151/251A

Spring 2024

Digital Design and Integrated Circuits

Instructor:

Wawrzynek

Lecture 14 - Exam1 Review


Announcements

- ❑ **Midterm Exam 6-9PM**
 - ❑ *Latimer 120 (alternate seating)*
 - ❑ *Exam covers Lectures 1 - 10 and HW 1 - 6 (Through CMOS circuits)*
 - ❑ *One double sided handwritten sheet of paper allowed. No calculators.*
 - ❑ *Neatness counts! Bring a ruler to help draw diagrams.*
- ❑ Homework solutions posted through HW 6
- ❑ No homework due today
- ❑ HW7 posted, due next Monday.

Review with sample slides

- ❑ Do not study only the following slides. These are just representative of what you need to know.
- ❑ Go back and study the entire lecture.


Moore's Law – 2x transistors per 1-2 yr

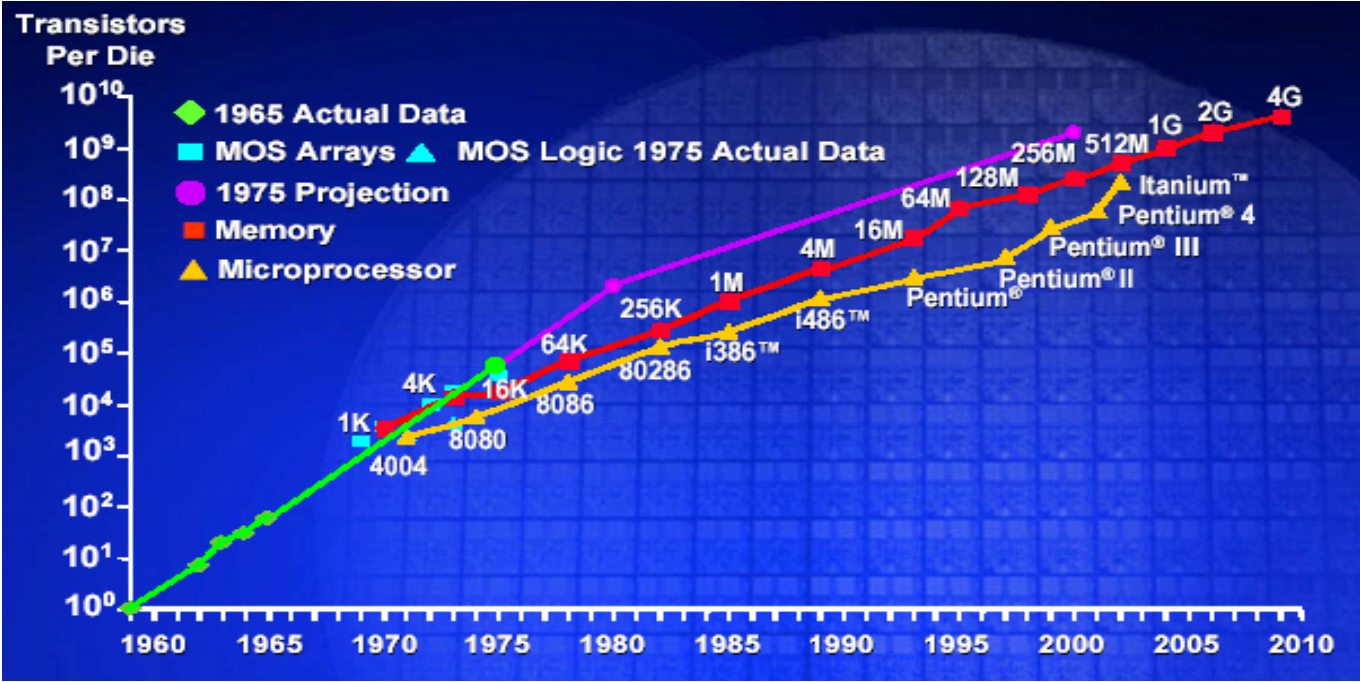

Dennard

Scaling

 Things we do: scale dimensions, doping, V_{dd} .



What we get:

κ^2 as many transistors at the same power density!


Whose gates switch κ times faster!

TABLE I
SCALING RESULTS FOR CIRCUIT PERFORMANCE

Device or Circuit Parameter	Scaling Factor
Device dimension t_{ox}, L, W	$1/\kappa$
Doping concentration N_a	κ
Voltage V	$1/\kappa$
Current I	$1/\kappa$
Capacitance $\epsilon A/t$	$1/\kappa$
Delay time/circuit VC/I	$1/\kappa$
Power dissipation/circuit VI	$1/\kappa^2$
Power density VI/A	1

Power density scaling ended in 2003 (Pentium 4: 3.2GHz, 82W, 55M FETs).

Design Space & Optimality

 

Cost

□ Non-recurring engineering (NRE) costs

□ Cost to develop a design (product) - *people, tools, masks*

- Amortized over all units shipped
- E.g. \$20M in development adds \$.20 to each of 100M units

aka recurring cost

aka NRE cost

□ Recurring costs


- Cost to manufacture, test and package a unit
- Processed wafer cost is ~\$10k (around 16nm node) which yields:
 - 50-100 large FPGAs or GPUs
 - 200 laptop CPUs
 - >1000 cell phone SoCs

$$\text{cost per IC} = \text{variable cost per IC} + \frac{\text{fixed cost}}{\text{volume}}$$

$$\text{variable cost} = \frac{\text{cost of die} + \text{cost of die test} + \text{cost of packaging}}{\text{final test yield}}$$

Relationship Among Representations

 - * Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.




How do we convert from one to the other?




Logic Gate Restoration

 Example (look at 1-input gate, to keep it simple):

- ❑ Inverter acts like a “non-linear” amplifier
- ❑ The non-linearity is critical to restoration
- ❑ Other logic gates act similarly with respect to input/output relationship.



Idealize Inverter

   


*Actual Inverter
voltage transfer
characteristic (VTC)*

Register Transfer Level Abstraction (RTL)

Any synchronous digital circuit can be represented with:

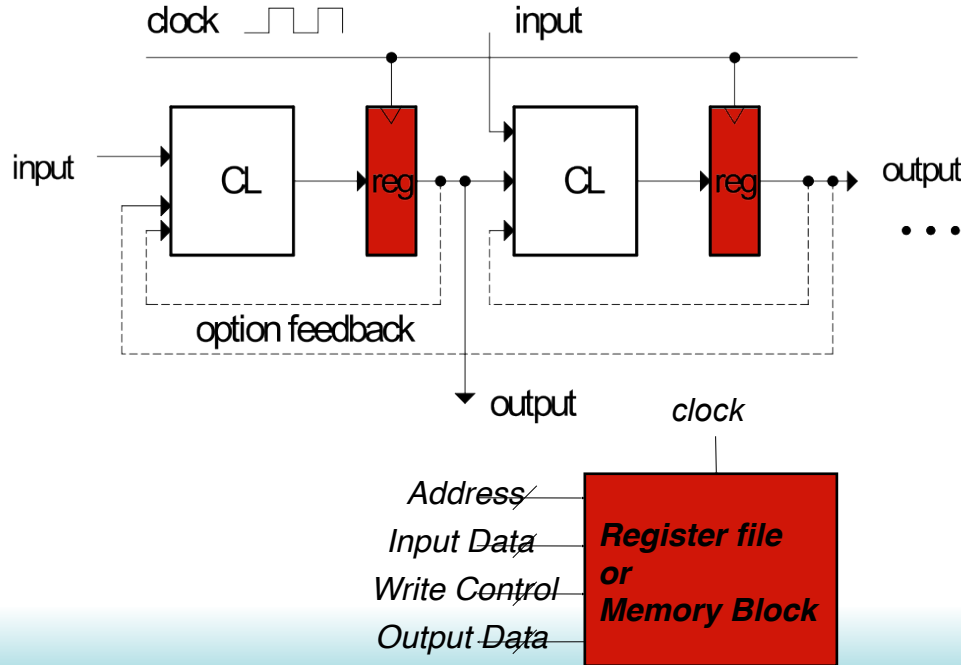- Combinational Logic Blocks (CL), plus
- State Elements (registers or memories)



- State elements are mixed in with CL blocks to control the flow of data.

- Sometimes used in large groups by themselves for “long-term” data storage.

Implementation Alternative Summary

Full-custom:	All circuits/transistors layouts optimized for application.
Standard-cell (ASIC):	Small function blocks/"cells" (gates, FFs) automatically placed and routed.
Gate-array (structured ASIC):	Partially prefabricated wafers with arrays of transistors customized with metal layers or vias.
FPGA:	Prefabricated chips customized with loadable latches or fuses.
Microprocessor:	Instruction set interpreter customized through software.
Domain Specific Processor:	Special instruction set interpreters (ex: DSP, NP, GPU, TPU).

What are the important metrics of comparison?

Hardware Description Languages

- Basic Idea:
 - Language constructs describe circuits with two basic forms:
 - **Structural descriptions:** connections of components. Nearly one-to-one correspondence to with schematic diagram.
 - **Behavioral descriptions:** use high-level constructs (similar to conventional programming) to describe the circuit function.
- Originally invented for simulation.
 - “logic synthesis” tools exist to automatically convert to gate level representation.
 - High-level constructs greatly improves designer productivity.
 - However, this may lead you to falsely believe that hardware design can be reduced to writing programs*

“Structural” example:

```
Decoder(output x0,x1,x2,x3;  
inputs a,b)  
{  
    wire abar, bbar;  
    inv(bbar, b);  
    inv(abar, a);  
    and(x0, abar, bbar);  
    and(x1, abar, b );  
    and(x2, a, bbar);  
    and(x3, a, b );  
}
```

“Behavioral” example:

```
Decoder(output x0,x1,x2,x3;  
inputs a,b)  
{  
    switch [a b]  
        case 00: [x0 x1 x2 x3] = 0x8;  
        case 01: [x0 x1 x2 x3] = 0x4;  
        case 10: [x0 x1 x2 x3] = 0x2;  
        case 11: [x0 x1 x2 x3] = 0x1;  
    endswitch;  
}
```

Warning: this is a fake HDL!

*New tools and languages exist for this - called “high level synthesis”.

Review - Ripple Adder Example


```

module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

  assign r = a ^ b ^ ci;
  assign co = a&ci + a&b + b&cin;

endmodule

```

 


```

module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

  wire c1, c2, c3;
  FullAdder
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );

endmodule

```

 

Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

```
module Adder(A, B, R);  
    parameter N = 4;  
    input [N-1:0] A;  
    input [N-1:0] B;  
    output [N:0] R;  
    wire [N:0] C;  
  
    genvar i;  
    generate  
        for (i=0; i<N; i=i+1) begin:bit  
            FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));  
        end  
    endgenerate  
  
    assign C[0] = 1'b0;  
    assign R[N] = C[N];  
endmodule
```

Declare a parameter with default value.

Note: this is not a port. Acts like a “synthesis-time” constant.

Replace all occurrences of “4” with “N”.

variable exists only in the specification - not in the final circuit.

Keyword that denotes synthesis-time operations


For-loop creates instances (with unique names)

```
Adder adder4 ( ... );  
Adder #(.N(64))  
adder64 ( ... );
```


Overwrite parameter N at instantiation.

EECS151 Registers

 - ❑ All registers are “N” bits wide - the value of N is specified at instantiation
- ❑ All positive edge triggered.



 
```
module REGISTER(q, d, clk);  
    parameter N = 1;
```




```
module REGISTER_CE(q, d, ce, clk);  
    parameter N = 1;
```

 On the rising clock edge if clock enable (ce) is 0 then the register is disabled (it's state will not be changed).



```
module REGISTER_R(q, d, rst, clk);  
    parameter N = 1;  
    parameter INIT = {N{1'b0}};
```

 On the rising clock edge if reset (rst) is 1 then the state is set to the value of INIT. Default INIT value is all 0's.




```
module REGISTER_R_CE(q, d, rst, ce, clk);  
    parameter N = 1;  
    parameter INIT = {N{1b'0}};
```

Reset (rst) has priority over clock enable (ce).


4-bit wrap-around counter

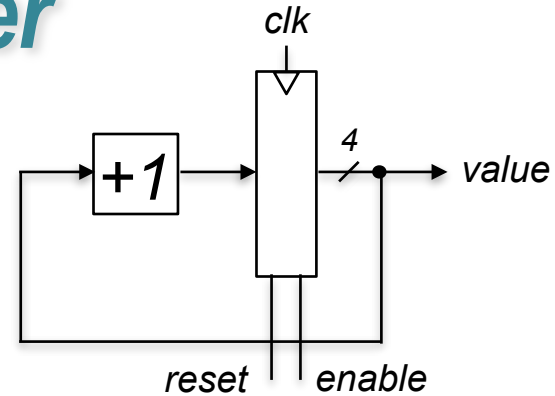0, 1, 2, 3, 4, 5, 6, 7, 8,
9, 10, 11, 12, 13, 14,
15, 0, 1, ...



```
module counter(value, enable, reset, clk);  
    output [3:0] value;  
    input        enable, reset, clk;  
    wire [3:0]  next;  
    REGISTER_R #(4) state (.q(value), .d(next), .rst(reset), .clk(clk));  
    assign next = value + 1;  
endmodule // counter
```


Example - Parallel to Serial Converter

 

Specifies the muxing with "rotation"

Instantiates a register (flip-flops) to be rewritten every cycle

connect output

```
module ParToSer(ld, X, out, clk);  
  input [3:0] X;  
  input ld, clk;  
  output out;
```

```
  wire [3:0] Q;  
  wire [3:0] NS;
```

```
  assign NS =  
    (ld) ? X : {Q[0], Q[3:1]};
```

```
  REGISTER state #(4)  
    (.q(Q), .d(NS), .clk(clk));
```

```
  assign out = Q[0];
```


```
endmodule
```

Verilog to ASIC layout flow


- “push-button” approach

```
module adder64 (a, b, sum);  
  input [63:0] a, b;  
  output [63:0] sum;  
  
  assign sum = a + b;  
endmodule
```


After
Synthesis

 

After Routing

 


After
Placement

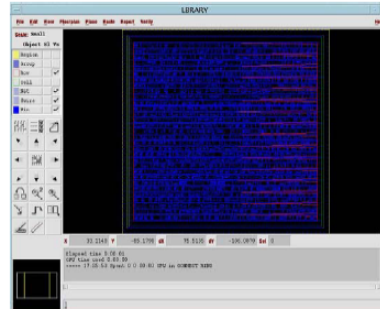

FPGA Overview

 - Basic structure: two-dimensional array of logic blocks and flip-flops with a means for the user to configure (program):
 1. the interconnection between the logic blocks,
 2. the function of each block.



Simplified version of FPGA internal architecture


User Programmability

❑ Latches are used to:

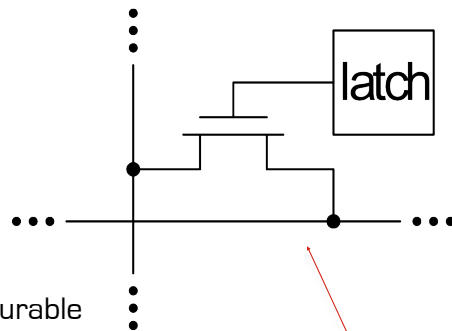1. control a switch to make or break cross-point connections in the interconnect
2. define the function of the logic blocks
3. set user options:
 - within the logic blocks
 - in the input/output blocks
 - global reset/clock

❑ “Configuration bit stream” is loaded under user control

- Latch-based (Xilinx, Intel/Altera, ...)




- + reconfigurable
- volatile
- relatively large.


MOSFET used as a “switch”

4-LUT Implementation

 - ❑ LUT size named by number of inputs
- ❑ n-bit LUT is implemented as a $2^n \times 1$ memory:
 - inputs choose one of 2^n memory locations.
 - memory locations (latches) are loaded with values from user's configuration bit stream.
 - Inputs to mux control are the LUT inputs.
- ❑ Result is a general purpose "logic gate".
 - n-LUT can implement any function of n inputs!




Example Partition, Placement, and Route

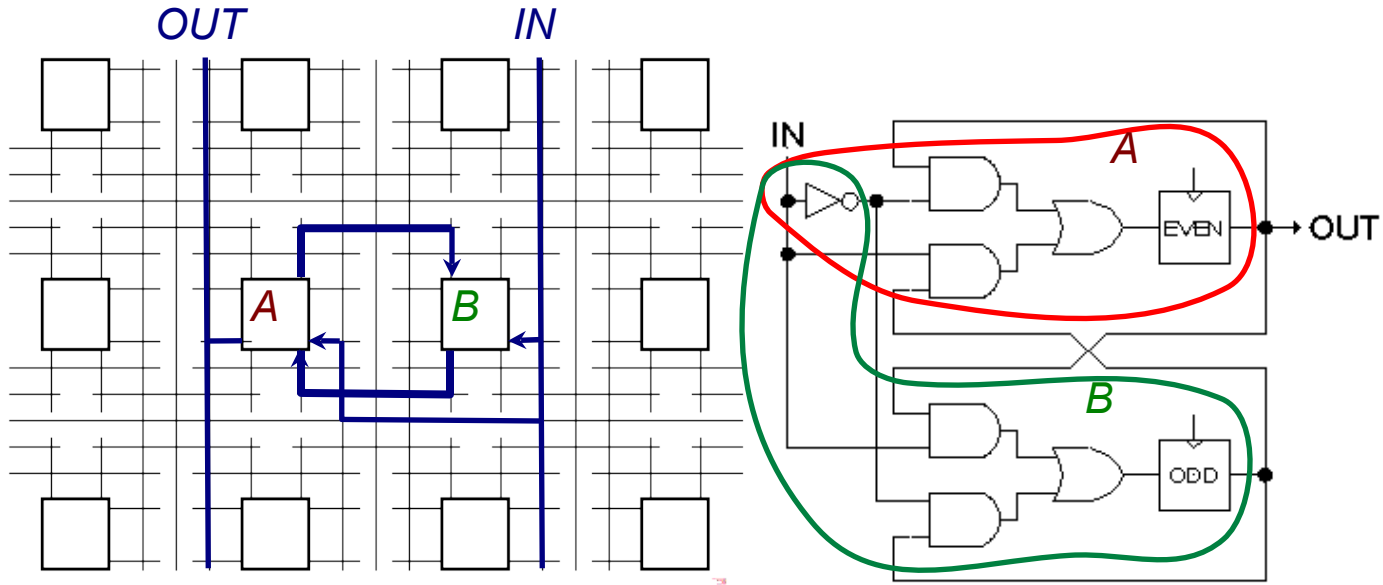

Two partitions. Each has single output, no more than 4 inputs, and no more than 1 flip-flop. In this case, inverter goes in both partitions.

Note: (with 4-LUTs) the partition can be arbitrarily large as long as it has not more than 4 inputs and 1 output, and no more than 1 flip-flop.

FPGA versus ASIC

 

- **ASIC:** Higher NRE costs (10's of \$M). Relatively Low cost per die (10's of \$ or less).
- **FPGAs:** Low NRE costs. Relatively low silicon efficiency \Rightarrow high cost per part (> 10's of \$ to 1000's of \$).
- **Cross-over volume** from cost effective FPGA design to ASIC was often in the 100K range.

Some Laws of Boolean Algebra

Duality: A dual of a Boolean expression is derived by interchanging OR and AND operations, and 0s and 1s (literals are left unchanged).

$$\{F(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)\}^D = \{F(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)\}$$

Any law that is true for an expression is also true for its dual.

Operations with 0 and 1:

$$\begin{array}{ll} \mathbf{x + 0 = x} & \mathbf{x * 1 = x} \\ \mathbf{x + 1 = 1} & \mathbf{x * 0 = 0} \end{array}$$

Idempotent Law:

$$\mathbf{x + x = x} \quad \mathbf{x * x = x}$$

Involution Law:

$$\mathbf{(x')' = x}$$

Laws of Complementarity:

$$\mathbf{x + x' = 1} \quad \mathbf{x * x' = 0}$$

Commutative Law:

$$\mathbf{x + y = y + x} \quad \mathbf{x * y = y * x}$$

Algebraic Simplification

$$\begin{aligned} \text{Cout} &= a'bc + ab'c + abc' + abc \\ &= a'bc + ab'c + abc' + abc + abc \\ &= a'bc + abc + ab'c + abc' + abc \\ &= (a' + a)bc + ab'c + abc' + abc \\ &= (1)bc + ab'c + abc' + abc \\ &= bc + ab'c + abc' + abc + abc \\ &= bc + ab'c + abc + abc' + abc \\ &= bc + a(b' + b)c + abc' + abc \\ &= bc + a(1)c + abc' + abc \\ &= bc + ac + ab(c' + c) \\ &= bc + ac + ab(1) \\ &= bc + ac + ab \end{aligned}$$

Canonical Forms

- Standard form for a Boolean expression - unique algebraic expression directly from a true table (TT) description.
- Two Types:
 - * **Sum of Products (SOP)**
 - * **Product of Sums (POS)**
- Sum of Products [disjunctive normal form, minterm expansion]. Example:

Minterms	a	b	c	f	f'
a'b'c'	0	0	0	0	1
a'b'c	0	0	1	0	1
a'bc'	0	1	0	0	1
a'bc	0	1	1	1	0
ab'c'	1	0	0	1	0
ab'c	1	0	1	1	0
abc'	1	1	0	1	0
abc	1	1	1	1	0

One product (and) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$





$$f' = a'b'c' + a'b'c + a'bc'$$

(enumerate all the ways the function could evaluate to 1)

What is the cost?


Karnaugh Map Method

    - Adjacent groups of 1's represent product terms




Multi-level Combinational Logic

 Another Example: $F = abc + abd + a'c'd' + b'c'd'$



let $x = ab$ $y = c+d$

 

$$f = xy + x'y'$$

Incorporates fanout.

No convenient hand methods exist for multi-level logic simplification:





a) CAD Tools use sophisticated algorithms and heuristics

Guess what? These problems tend to be NP-complete

b) Humans and tools often exploit some special structure (example adder)

NAND-NAND & NOR-NOR Networks



□ Mapping from AND/OR to NAND/NAND

    

Finite State Machines (FSMs)

FSMs:

  
- Can model behavior of any sequential circuit
- Useful representation for designing sequential circuits
- As with all sequential circuits: output depends on present *and* past inputs
 - effect of past inputs represented by the current *state*
- Behavior is represented by **State Transition Diagram**:
 - traverse one edge per clock cycle.



By-hand Design Process (b)

State Transition Table:

<i>present state</i>	<i>OUT</i>	<i>IN</i>	<i>next state</i>
<i>EVEN</i>	<i>0</i>	<i>0</i>	<i>EVEN</i>
<i>EVEN</i>	<i>0</i>	<i>1</i>	<i>ODD</i>
<i>ODD</i>	<i>1</i>	<i>0</i>	<i>ODD</i>
<i>ODD</i>	<i>1</i>	<i>1</i>	<i>EVEN</i>

 

Invent a code to represent states:

Let 0 = EVEN state, 1 = ODD state


<i>present state (ps)</i>	<i>OUT</i>	<i>IN</i>	<i>next state (ns)</i>
<i>0</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>0</i>	<i>0</i>	<i>1</i>	<i>1</i>
<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>
<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>

Derive logic equations
from table (how?):

$$OUT = PS$$

$$NS = PS \text{ xor } IN$$

FSM CL block rewritten

 


```
always @* * for sensitivity list
begin
  next_state = IDLE; Normal values: used unless specified below.
  out = 1'b0;
  case (state)
    IDLE : if (in == 1'b1) next_state = S0;
    S0    : if (in == 1'b1) next_state = S1;
    S1    : begin
              out = 1'b1;
              if (in == 1'b1) next_state = S1;
            end
    default: ;
  endcase
end
Endmodule
```

Within case only need to specify exceptions to the normal values.


Note: The use of "blocking assignments" allow signal values to be "rewritten", simplifying the specification.

FSM Moore and Mealy Implementation Review


Moore Machine

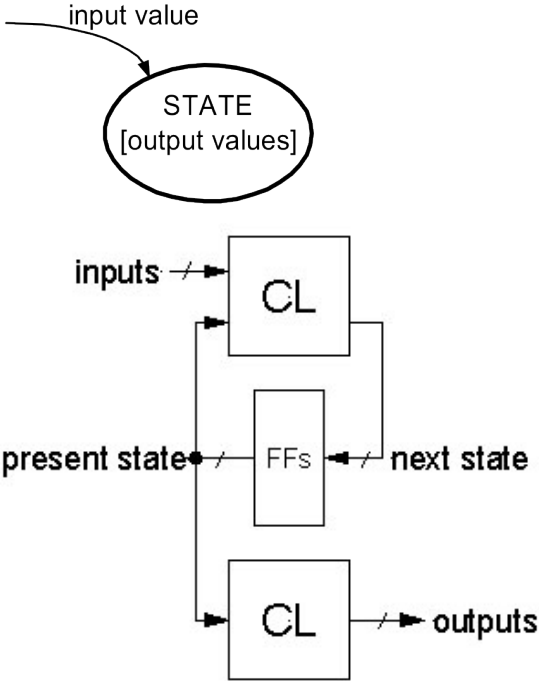


Mealy Machine

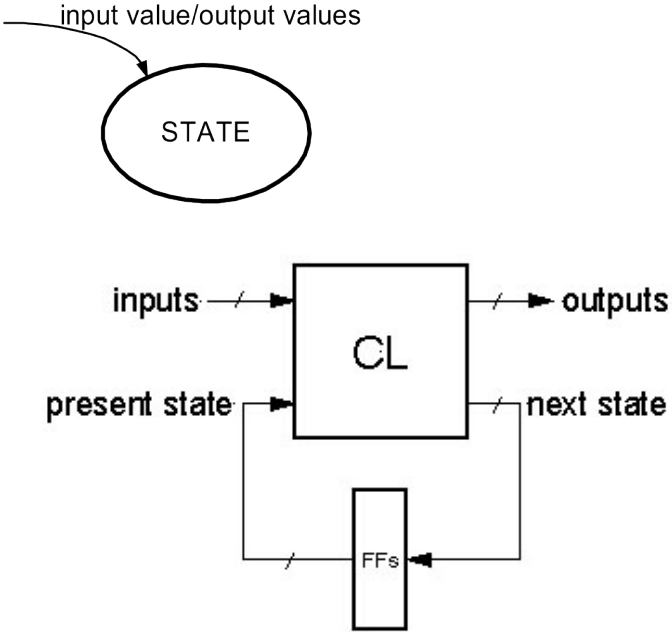


One-hot encoded combination lock

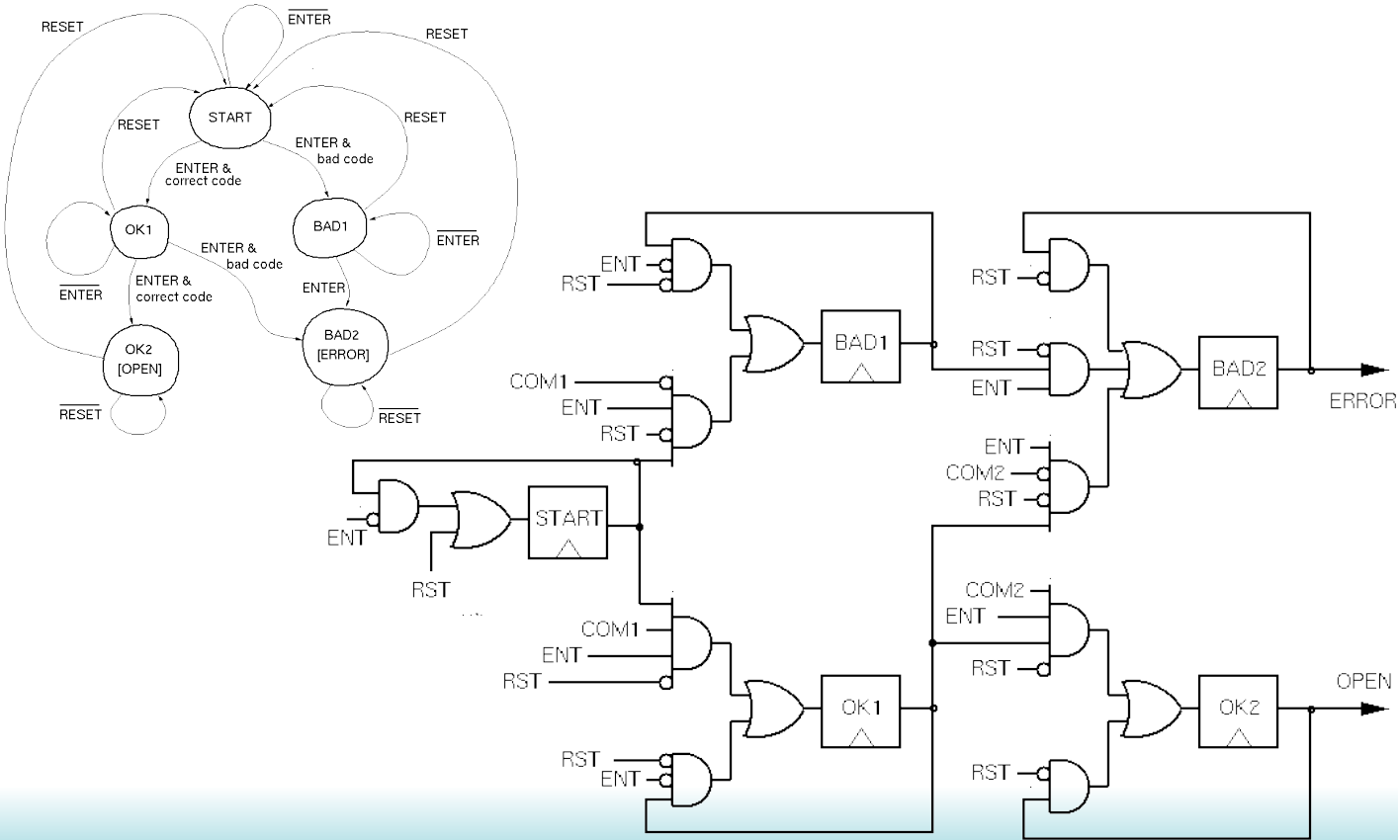

Final product ...

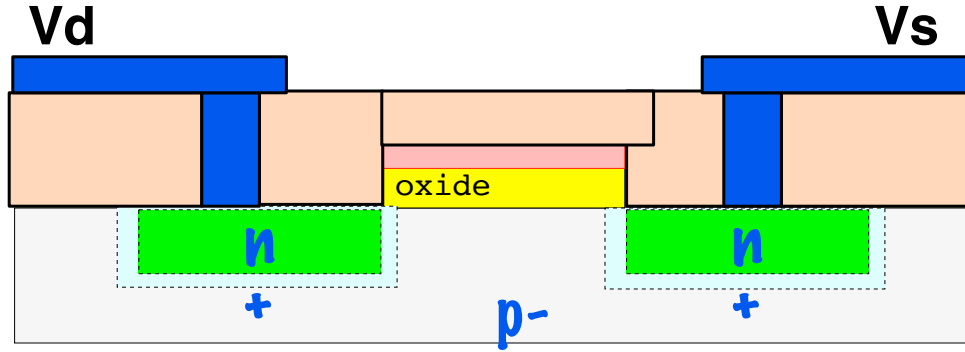

Top-down view:

 


"The planar process"

Jean Hoerni,
Fairchild
Semiconductor
1958



Physical Layout

 
- ❑ How do transistor circuits get “laid out” as geometry?
- ❑ What circuit does a physical layout implement?
- ❑ Where are the transistors and wires and contacts and vias?



Complex CMOS Gate


$$\text{OUT} = \overline{D + A \cdot (B + C)}$$
 
$$\text{OUT} = \overline{D \cdot A + B \cdot C}$$




4-to-1 Transmission-gate Mux

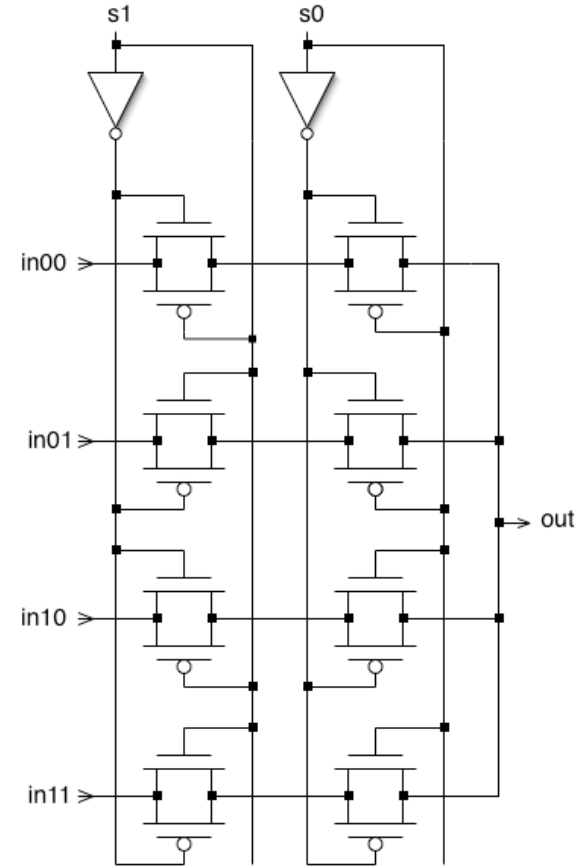
- ❑ The series connection of pass-transistors in each branch effectively forms the AND of s_1 and s_0 (or their complement).
- ❑ Compare cost to logic gate implementation



Tri-state Buffers

 


Variations:

 


OE	IN	OUT
0	-	Z
1	0	1
1	1	0

Inverting buffer

 


OE	IN	OUT
0	0	0
0	1	1
1	-	Z

Inverted enable

 

transmission gate useful in implementation

Positive edge-triggered flip-flop

 

A flip-flop “samples” on the positive clock-edge, and then “holds” value.

