

EECS 151/251A

Spring 2024

Digital Design and Integrated Circuits

Instructor:


John Wawrzynek

**Lecture 16:
Memory Circuits
and Blocks**

Announcements

- ❑ Project spec



 

Outline

SRAM

DRAM

Memory Blocks

Multi-ported RAM

Combining Memory blocks

FIFOs

FPGA memory blocks

Caches

Memory Blocks in the FPGA Project

First, Some Memory Classifications:


- Hardwired (Read-only-memory- ROM)
- Programmable
 - *Volatile*
 - SRAM - uses positive feedback (and restoration) to hold state
 - DRAM - uses capacitive charge (only) to hold state
 - *Non-volatile*
 - Persistent state without power supplied
 - Ex: Flash Memory

Memory Circuits


Volatile Storage Mechanisms

These circuits represent the principles of storing a bit:

Static - feedback

 


Dynamic - charge

 


Circuit details differ, depending on application.

Generic Memory Block Architecture

 - ❑ **Word lines** used to select a row for reading or writing
- ❑ **Bit lines** carry data to/from periphery
- ❑ **Core aspect ratio** keep close to 1 to help balance delay on word line versus bit line
- ❑ **Address bits** are divided between the two decoders
- ❑ **Row decoder** used to select word line
- ❑ **Column decoder** used to select one or more columns for input/output of data



 Storage cell could be either static or dynamic




Memory - SRAM


- ❑ Used for on-chip memories. Caches, large register files, input/output buffers, ...
- ❑ Compatible with logic processes.

Memory Cells


 
Complementary data values are written (read) from two sides



Cells stacked in 2D to form memory core.

 


6T-SRAM — Older Layout Style

 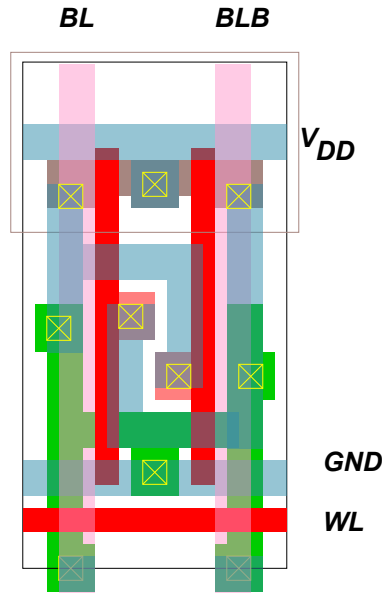


V_{DD} and GND: in M1(blue)
Bitlines: M2 (purple)
Wordline: poly-silicon (red)

Modern SRAM

□ ST/Philips/Motorola

 


Access Transistor

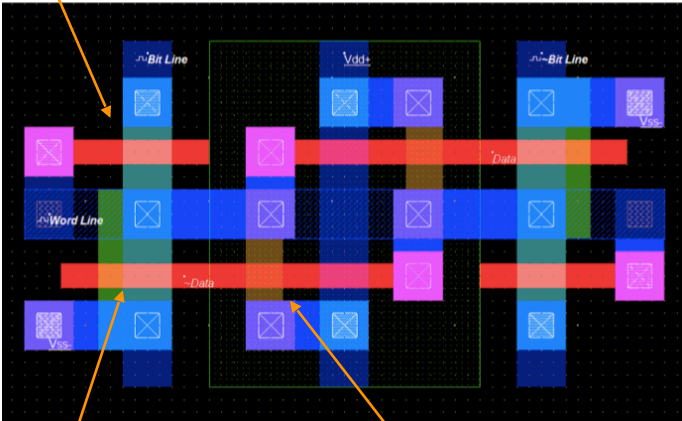


Pull down

Pull up

 

SRAM Operation - Read

 1. Bit lines are “pre-charged” to VDD
2. Word line is driven high (pre-charger is turned off)
3. Cell pulls-down one bit line
4. Differential sensing circuit on periphery is activated to capture value on bit lines.




During read \overline{Q} will get slightly pulled up when WL first goes high, but ...


- *But by sizing the transistors correctly, reading the cell will not destroy the stored value*

SRAM Operation - Write

 1. Column driver circuit on periphery differentially drives the bit lines
2. Word line is driven high (column driver stays on)
3. One side of cell is driven low, flips the other side




 For successful write the access transistor needs to overpower the cell pullup. The transistors are sized to allow this to happen.



Memory Periphery


On-chip Memory

 


ARM A5 Photo

Periphery

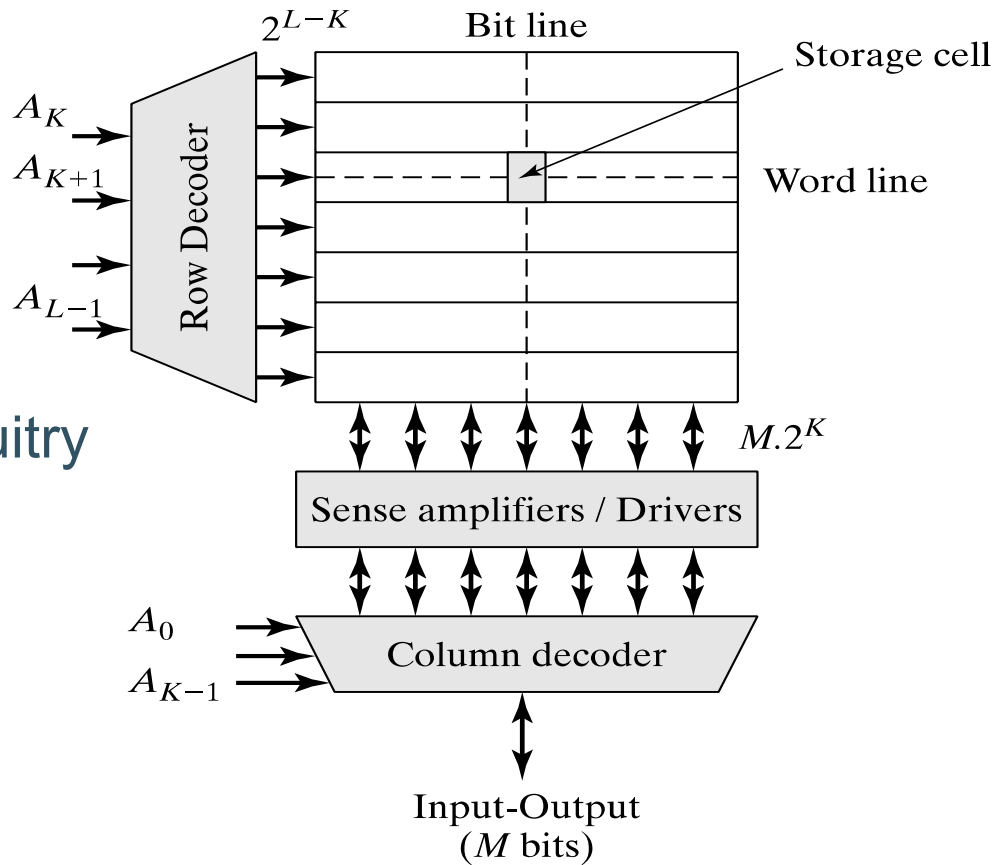- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry



Row Decoder

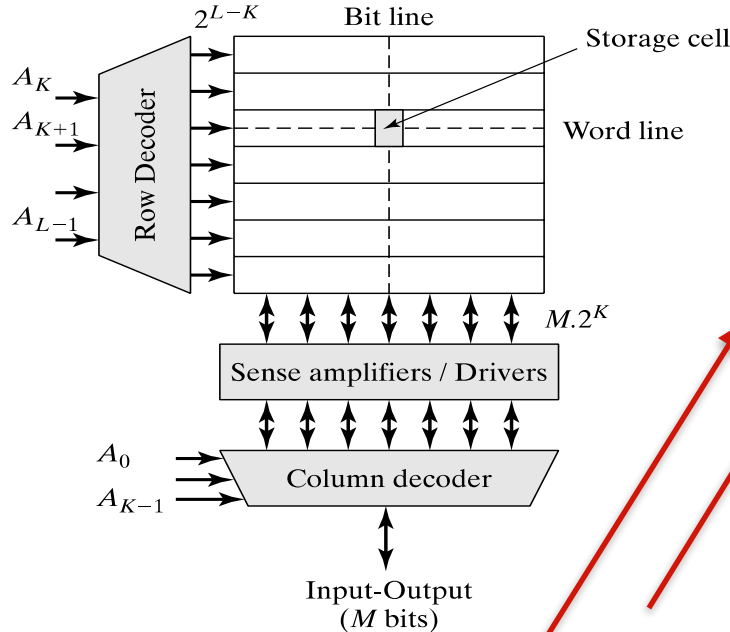

- L total address bits
- K for column decoding
- L-K for row decoding
- Row decoder expands L-K address lines into 2^{L-K} word lines
- M bits per word

□ Example: decoder for 8Kx8 memory block

- core arranged as 256x256 cells
- Need 256 AND gates, each driving one word line

each row has 32 8-bit words (8x32=256)

8K x 8 means 8K words of 8-bits each

In this case: L=13 total address bits ($2^L=8K$), K=5 ($2^K=32$), L-K=8 ($2^{L-K}=256$)

Row Decoders

(N)AND Decoder


$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$

NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$
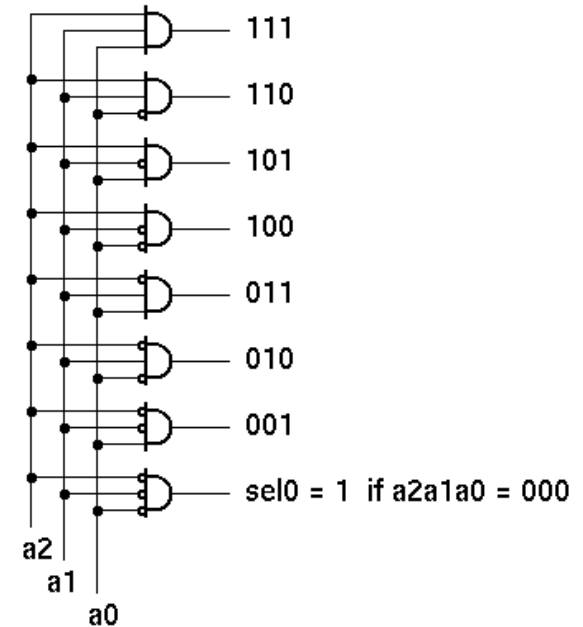
$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$



Collection of 2^{L-K} logic gates, but need to be dense and fast.

Naive solution would require $L-K$ input gates: *Too big to pitch match to storage cells and too slow.*


Predecoders

$\overline{a_5} \overline{a_4}$	$\overline{a_3} \overline{a_2}$	$\overline{a_1} \overline{a_0}$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} \overline{a_2}$	$\overline{a_1} a_0$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} \overline{a_2}$	$a_1 \overline{a_0}$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} \overline{a_2}$	$a_1 a_0$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} a_2$	$\overline{a_1} \overline{a_0}$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} a_2$	$\overline{a_1} a_0$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} a_2$	$a_1 \overline{a_0}$
$\overline{a_5} \overline{a_4}$	$\overline{a_3} a_2$	$a_1 a_0$
•		
•		
•		

$a_5 a_4 a_3 a_2$	$\overline{a_1} \overline{a_0}$
$a_5 a_4 a_3 a_2$	$\overline{a_1} a_0$
$a_5 a_4 a_3 a_2$	$a_1 \overline{a_0}$
$a_5 a_4 a_3 a_2$	$a_1 a_0$

- Use a single gate for each of the shared terms
 - E.g., from $a_1, \overline{a_1}, a_0, \overline{a_0}$ generate four signals:
 - $\overline{a_1} \overline{a_0}, \overline{a_1} a_0, a_1 \overline{a_0}, a_1 a_0$
- Do same for a_5, a_4, a_3, a_2
- In other words, we decode smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding


Predecoder and Decoder

 

Predecoders

Final Decoder

Column "Decoder"

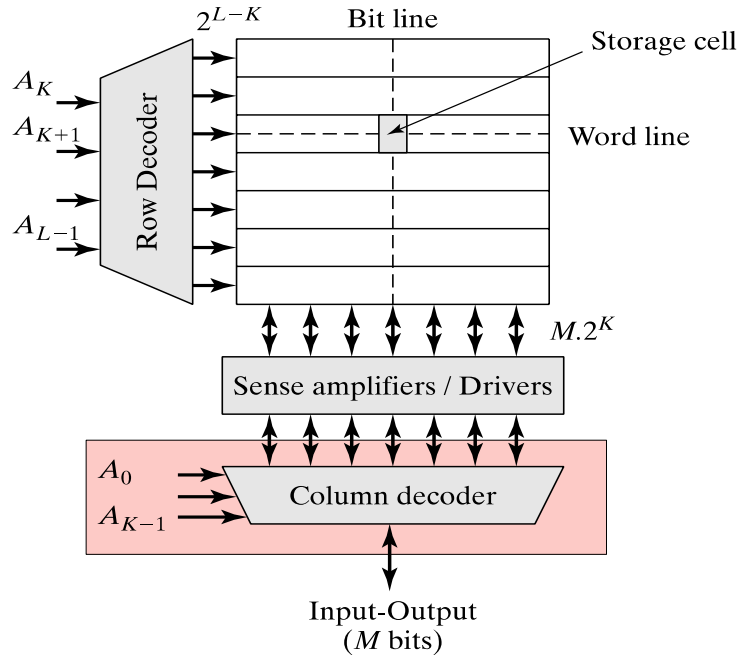


- ❑ Is basically a multiplexer
- ❑ Each row contains 2^K words each M bits wide.
- ❑ Bit of each of the 2^K are interleaved
 - ❑ ex: $K=2, M=8$



$d_7c_7b_7a_7d_6c_6b_6a_6d_5c_5b_5a_5d_4c_4b_4a_4d_3c_3b_3a_3d_2c_2b_2a_2d_1c_1b_1a_1d_0c_0b_0a_0$

4 interleaved words A, B, C, D

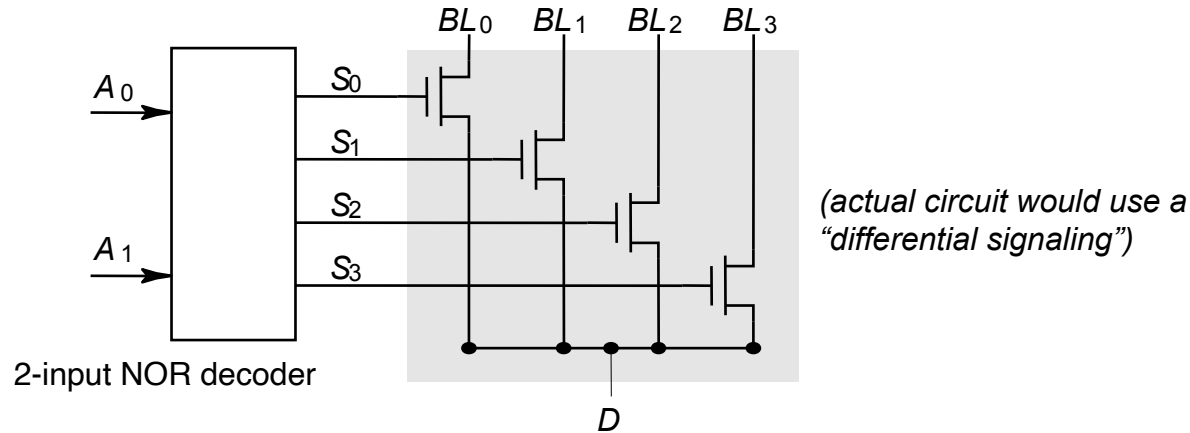4-input pass-transistor based Column Decoder (for read)



decoder shared across all $2^K \times M$ row bits

Advantages: speed (Only one extra transistor in signal path, share sense amp)

Sense Amplifiers Speed Reading


large Capacitance of bit lines

$$\tau_p \propto \frac{C \cdot \Delta V}{I_{av}}$$


make as small as possible

small

Idea: Use “Sense Amplifier”

 


Differential Sense Amplifier

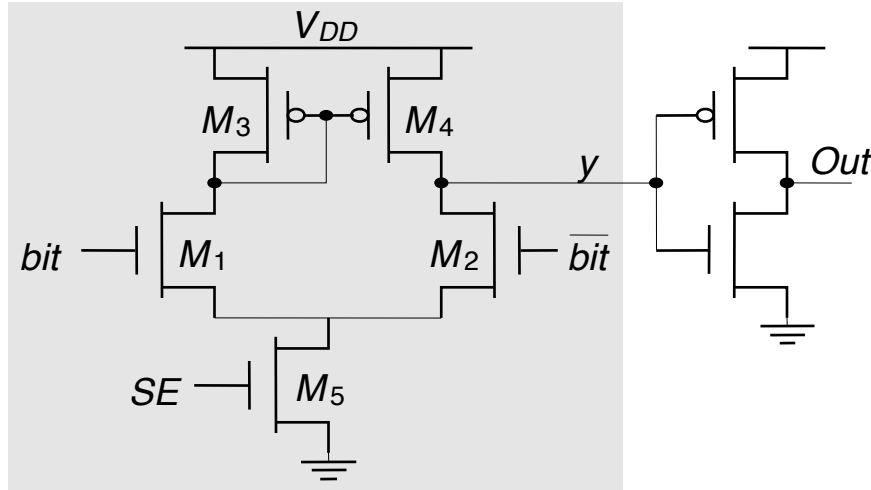

Classic Differential Amp structure - basis of opAmp

Differential Sensing – SRAM

 

(a) SRAM sensing scheme