

**EECS151/251A**

**Spring 2024**

**Digital Design and Integrated Circuits**

**Instructor:**


**John Wawrzynek**

**Lecture 24:**

**Clocks, Wrapup**
 
# Announcements

- ❑ Homework assignment 10 due today.
- ❑ HW 11 - final problem set - posted, due May 3.
- ❑ Final project checkoffs will be Wed of next week (RRR).
- ❑ Final reports will be due Wed at midnight of exam week.
- ❑ Apple has generously offered to provide prizes for the best projects this semester:
  - ❑ *The top ASIC project (2 students), & the top 3 FPGA projects (6 students)*
  - ❑ *The student can choose either an Apple Watch (SE GPS, 40mm) or Airpod Pro.*




## *Outline*

Clock non-idealities


Clock Distribution

Wrap up

 


## Synchronous Timing - Review

# Synchronous Timing

 


# Register Timing Parameters

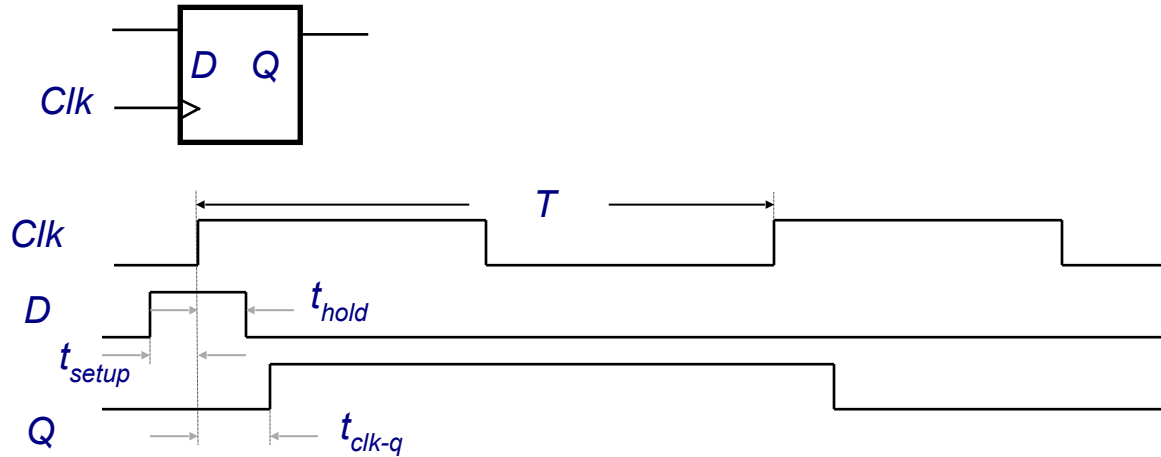

*Output delays can be different for rising and falling data transitions*


# Timing Constraints

 

$t_{clk-q,max}$   
 $t_{clk-q,min}$   
 $t_{setup}, t_{hold}$

$t_{logic,max}$   
 $t_{logic,min}$

# Timing Constraints

 


$t_{clk-q,max}$        $t_{logic,max}$   
 $t_{clk-q,min}$        $t_{logic,min}$   
 $t_{setup}, t_{hold}$

**Cycle time (max):**  $T_{clk} > t_{clk-q,max} + t_{logic,max} + t_{setup}$

 **Race margin (min):**  $t_{hold} < t_{clk-q,min} + t_{logic,min}$





## Clock Nonidealities

# Clock Nonidealities

## ❑ Clock skew: $t_{SK}$

- Time difference between the sink (receiving) and source (launching) clock edge; deterministic + random


## ❑ Clock jitter

- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term)  $t_{JS}$
- Long term  $t_{JL}$

## ❑ Variation of the pulse width


- Important for level sensitive clocking

*These create clock “uncertainty”*

 


# Clock Uncertainties

## Sources of clock uncertainty

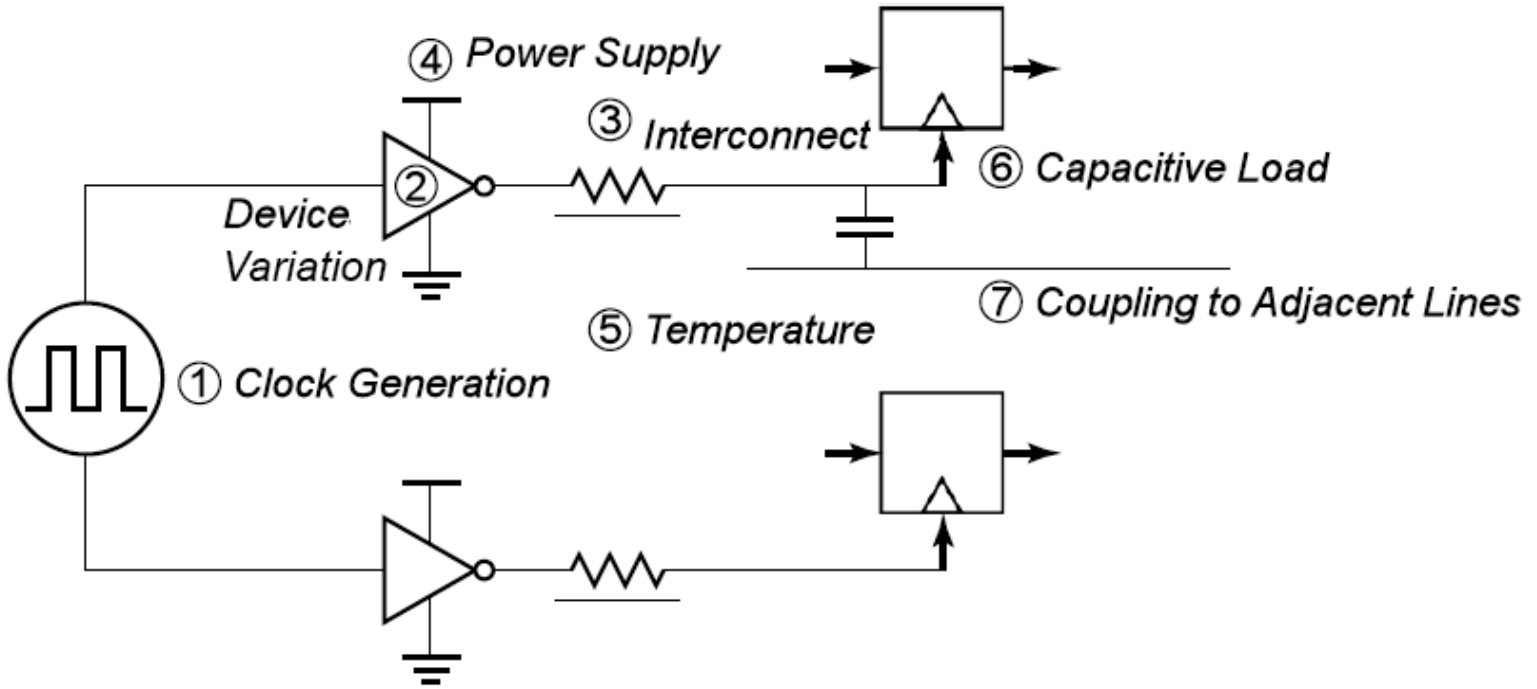


 
# Clock Skew and Jitter

- Both skew and jitter affect the effective cycle time and the hold time (race margin)



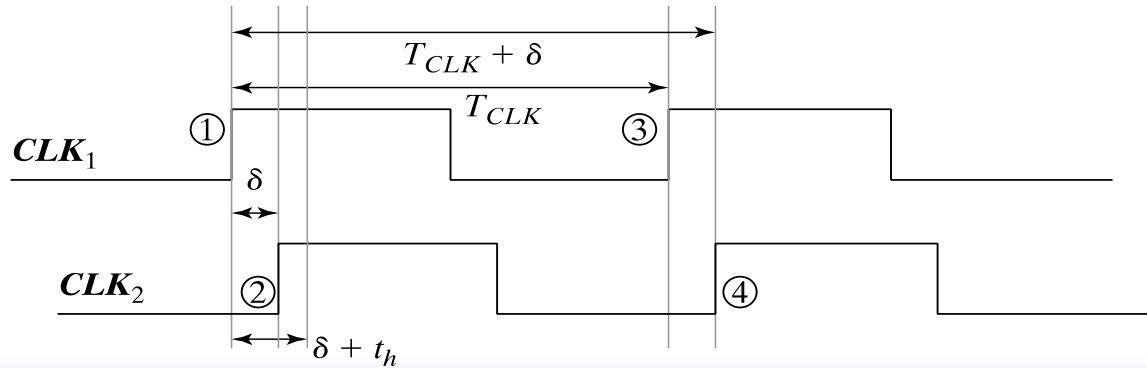
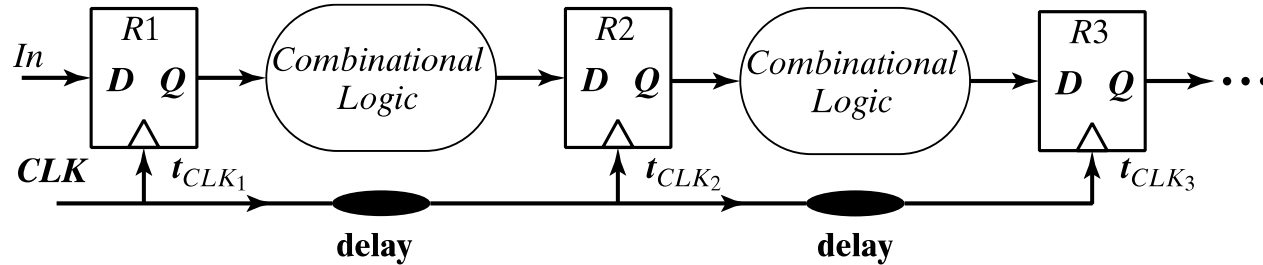
# Positive Skew

Launching edge arrives before the receiving edge



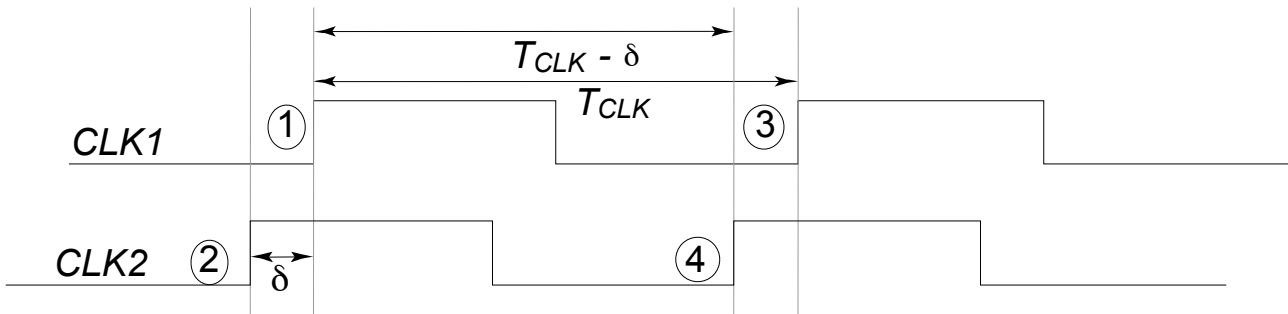 
# Negative Skew

Receiving edge arrives before the launching edge



# Timing Constraints

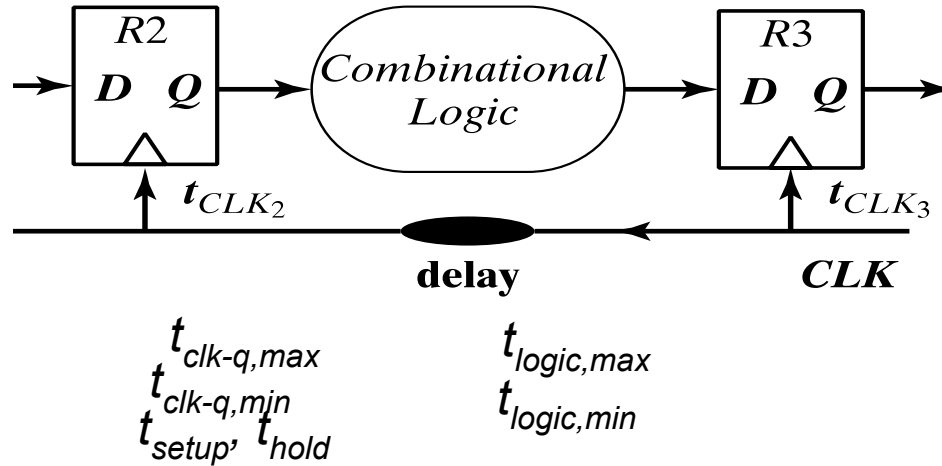


*Minimum cycle time:*

$$T_{\text{clk}} + \delta = t_{\text{clk-q,max}} + t_{\text{setup}} + t_{\text{logic,max}}$$

*Skew may be negative or positive*

# Timing Constraints

 

$t_{clk-q,max}$        $t_{logic,max}$   
 $t_{clk-q,min}$        $t_{logic,min}$   
 $t_{setup}, t_{hold}$

*Hold time constraint:*

$$t_{(clk-q,min)} + t_{(logic,min)} > t_{hold} + \delta$$

*Skew may be negative or positive*



# Clock Constraints in Edge-Triggered Systems

If launching edge is late and receiving edge is early, the data will not be too late if:

$$t_{clk-q,max} + t_{logic,max} + t_{setup} < T_{CLK} - t_{JS,1} - t_{JS,2} + \delta$$


Minimum cycle time is determined by the maximum delays through the logic


$$t_{clk-q,max} + t_{logic,max} + t_{setup} - \delta + 2t_{JS} < T_{CLK}$$

Skew can be either positive or negative

*Skew and Jitter are often expressed together as “uncertainty”*

# Datapath with Feedback

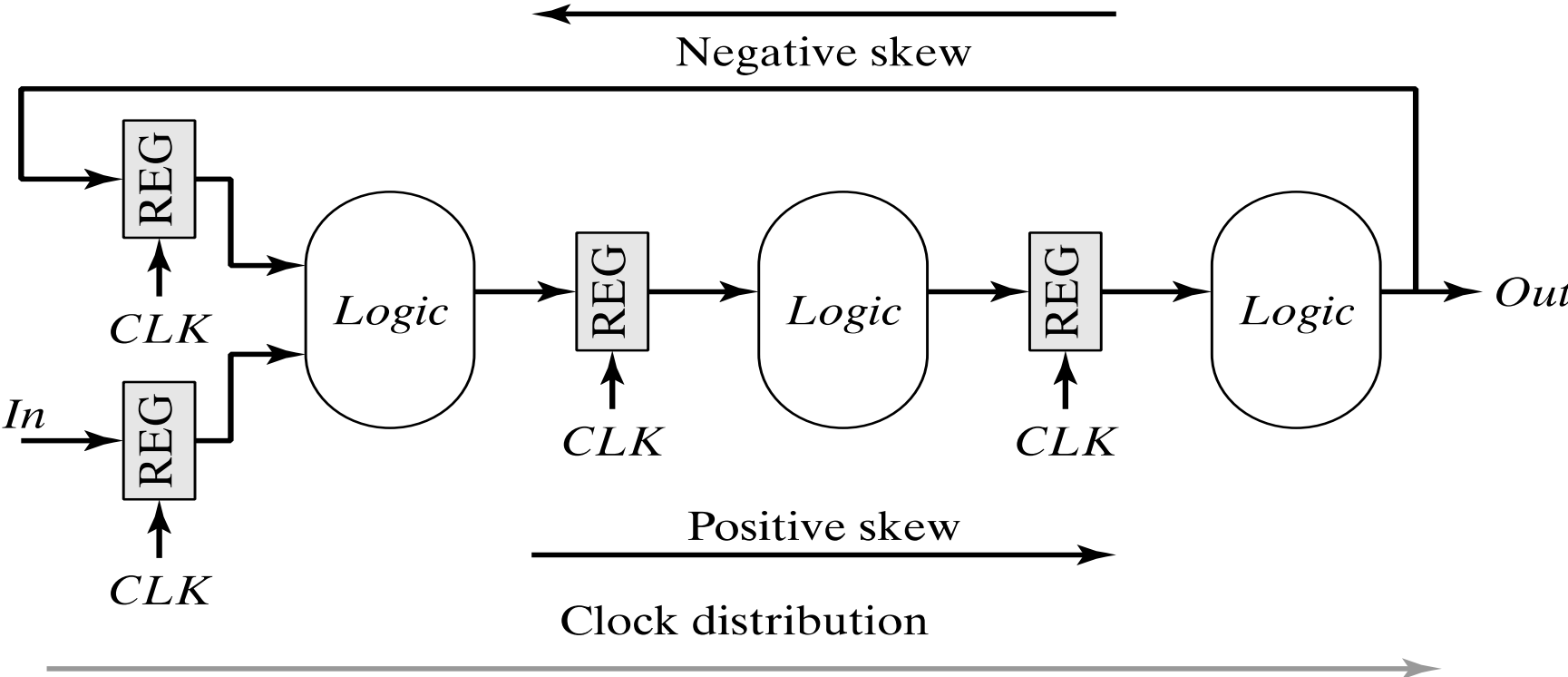

 


## Clock Distribution

# *Clock Distribution*



- Single clock generally used to synchronize all logic on the same chip (or region of chip)
  - Need to distribute clock over the entire region
  - While maintaining low skew/jitter
  - And without burning too much power
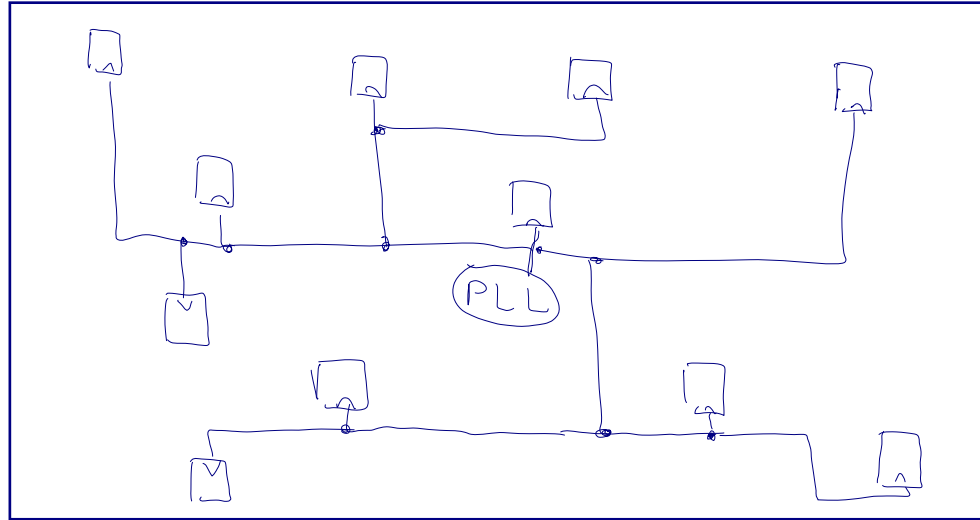
# Clock Distribution

- ❑ What's wrong with just routing wires to every point that needs a clock?




# H-Tree

  


Equal wire length/number of buffers to get to every location


# More realistic ASIC H-tree

 


*[Restle98]*

 



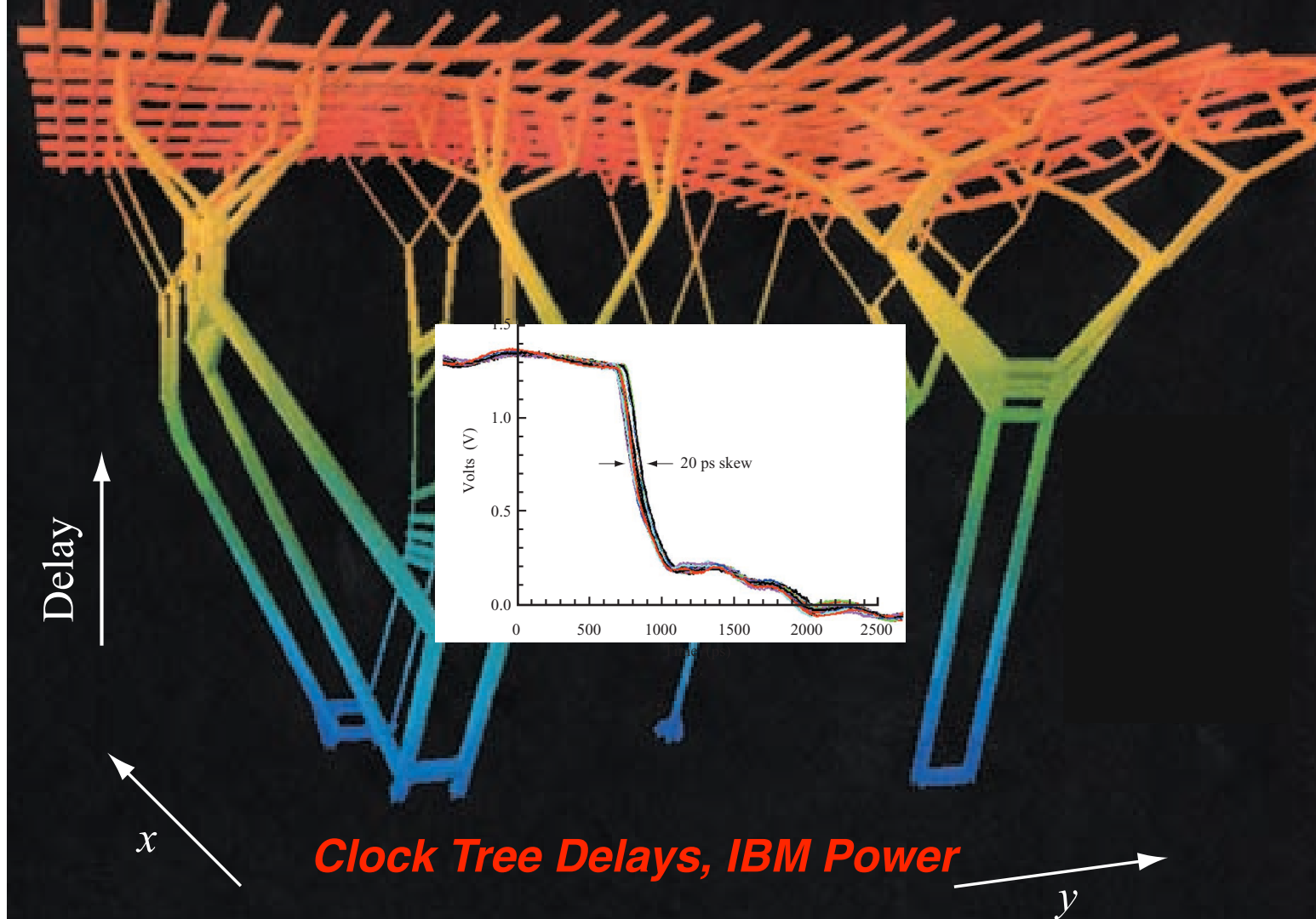

# Clocks have dedicated wires (low skew)

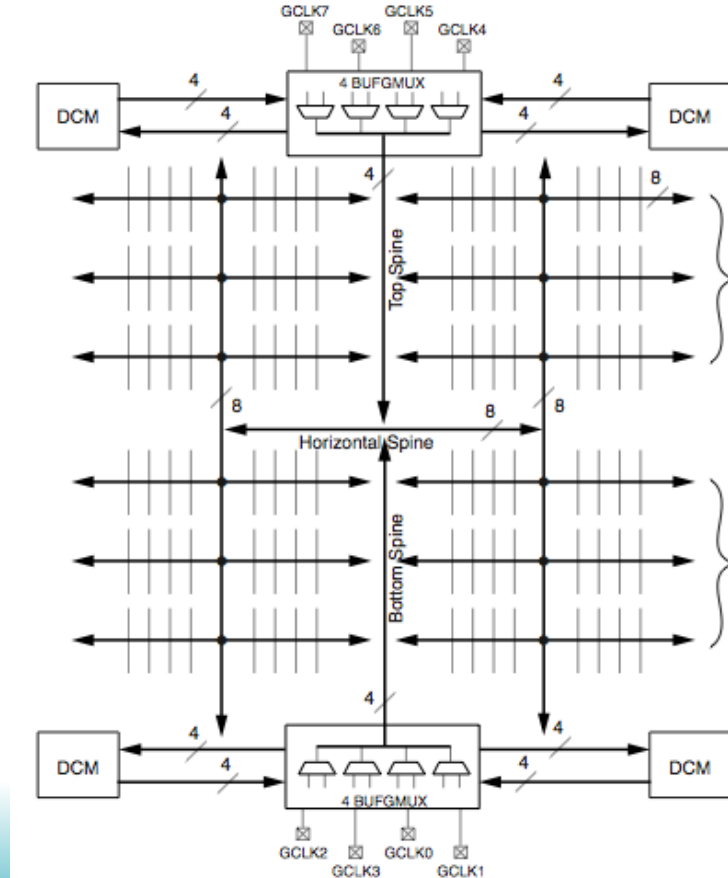

From: Xilinx Spartan 3 data sheet.  
Virtex is similar.

# ***End of Course Content***

# Why Study and Learn Digital Design?

- We expect that many of you will eventually be employed as designers.
  - **Digital design is not a spectator sport.** The only way to learn it, and to appreciate the issues, is to do it.
  - To a large extent, it comes with practice/experience (this course is just the beginning).
  - Another way to get better is to study other designs. Not time to do much of this during the semester, but a good practice for later.
- However, a significant percentage of our graduates will not be digital designers. What's in it for them?
  - Better manager of designers, marketers, field engineers, etc.
  - Better researcher/scientist/designer in related areas
    - Software engineers, fabrication process development, etc.

# *In What Context Will You be Designing?*


*Engineers learn so that they can build.  
Scientists build so that they can learn.*

- ❑ Electronic design is a critical tool for most areas of pure science:
  - Astrophysics – special electronics used for processing radio antenna signals.
  - Genomics – special processing architectures for DNA string matching.
  - In general - sensor processing, control, and number crunching.
  - Machine Learning now relies heavily on special hardware.
  - In some fields, computation has replaced experimentation – particle physics, world weather prediction (fluid dynamics).
- ❑ In computer engineering, prototypes often designed, implemented, and studied to “prove out” an idea. Common within universities and industrial research labs. Lessons learned and proven ideas often transferred to industry through licensing, technical communications, or startup companies.
  - RISC processors were first proved out at Berkeley and IBM Research
 
# Designs in Industry

- ❑ Of course, companies are the primary employer of designers. Provide some useful products to society or government and make a profit for the shareholders.
- ❑ Interesting recent shift
  - All software giants now have hardware design teams (embedded and chips)
  - Google, Amazon, Facebook, Microsoft, ...

Global Electronic System Production  
(\$1.62T, 2018F)



Source: IC Insights

# Top Ten Big Ideas from EECS151

1. **Modularity and Hierarchy** is an important way to describe and think about digital systems.
2. **Parallelism** is a key property of hardware systems and distinguishes them from serial software execution.
3. **Clocking and the use of state elements** (latches, flip-flops, and memories) control the flow of data.
4. **Cost/Performance/Power tradeoffs** are possible at all levels of the system design.
5. **Boolean Algebra** and other logic representations.
6. **Hardware Description Languages (HDLs) and Logic Synthesis** are a central tool for digital design.
7. **Datapath + Controller** is a effective design pattern.
8. **Finite State Machines** abstraction gives us a way to model any digital system – used for designing controllers.
9. **Arithmetic circuits** are often based on “long-hand” arithmetic techniques.
10. **FPGAs + ASICs** give us a convenient and flexible implementation technology.

# Important Topics We Didn't Cover

## ❑ Design Verification and Testing

- Industrial designers spend more than half their time testing and verifying correctness of their designs.
  - Some of this covered in the lab and guest lecture. Didn't cover rigorous testing procedures.
- Most industrial products are designed from the start for testability. Important for design verification and later for manufacturing test.
- Related: Fault modeling and fault tolerant design.

## ❑ Other High-level Optimization Techniques

- High-level Synthesis - now starting to catch on

## ❑ Other High-level Architectures: GPUs, video processing, network routers, ...


## ❑ Asynchronous Design



# *Most Closely Related Courses*

- ❑ CS152 Computer Architecture and Engineering
  - Design and Analysis of Microprocessors
  - Applies basic design concepts from EECS151
- ❑ EE251B Advanced Digital Integrated Circuits and Systems
  - Transistor-level design of ICs
  - More on Advanced ASIC Tool use
- ❑ EE 194/290C: The Tapeout Class
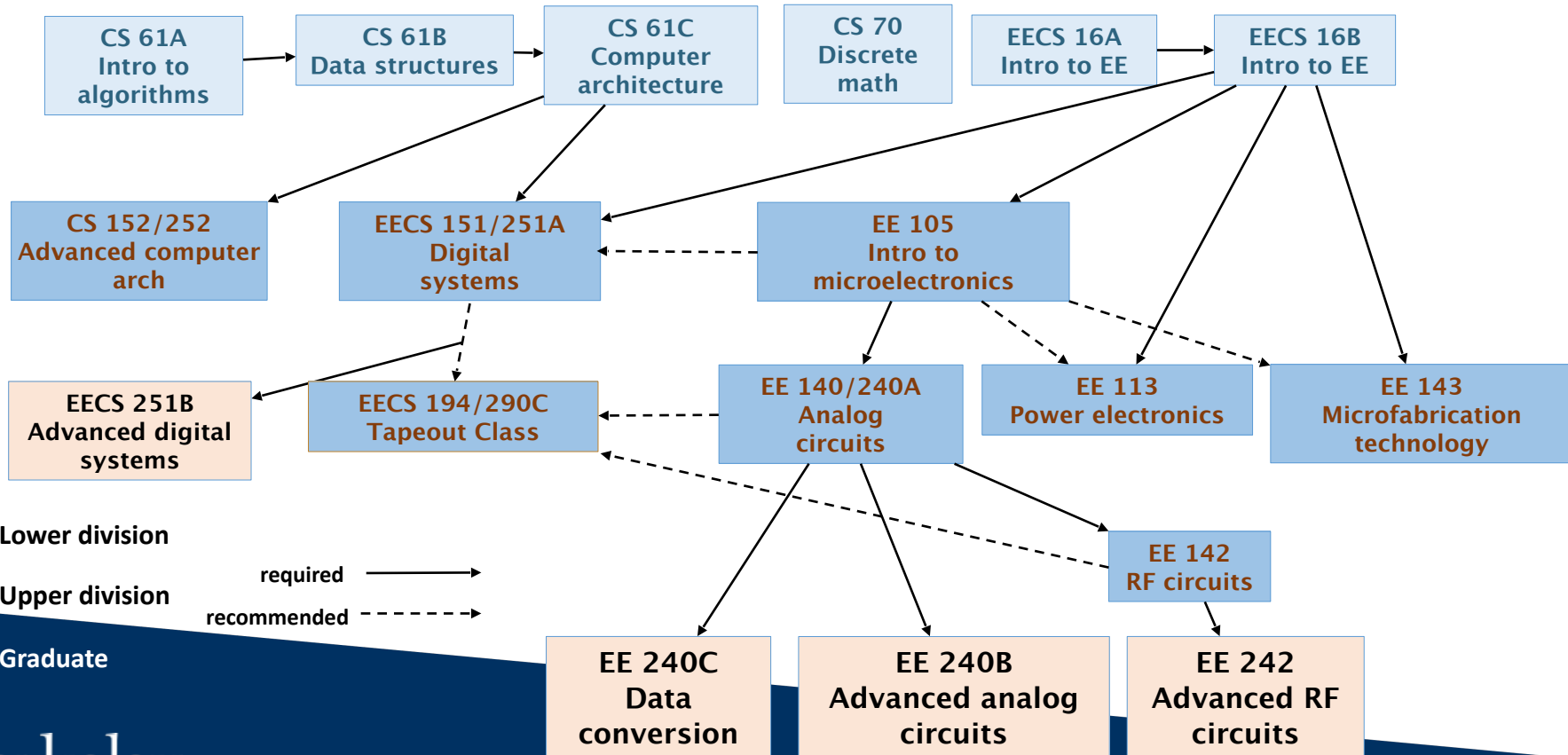
# EECS Circuits/Computer Hardware Course Flow Map



# Future Design Issues

- ❑ Automatic High-level synthesis (HLS) and optimization (with micro-architecture synthesis) and hardware/software co-design.
- ❑ Machine Learning and Digital Design:
  - Can ML techniques help us design better systems or do it more quickly?
- ❑ Current practice is “system on a chip” (SOC) design methodology:
  - Pre-designed subsystems (processor cores, bus controllers, memory systems, network interfaces, etc. ) connected with standard on-chip interconnect or bus.
  - Strong emphasis on “accelerators” for energy efficiency and performance.
- ❑ A number of alternatives to silicon VLSI have been proposed, including techniques based on:
  - Carbon nanotubes<sup>1</sup>, molecular electronics, quantum mechanics, and biological processes.
  - Quantum computing is on the horizon.<sup>2</sup>
  - How will these change the way we design systems?

1. In 2012, IBM produced a sub-10 nm [carbon nanotube transistor](#) that outperformed silicon on speed and power. "The superior low-voltage performance of the sub-10 nm CNT transistor proves the viability of nanotubes for consideration in future aggressively scaled transistor technologies", according to the abstract of the paper in [Nano Letters](#).

2. **McKinsey has estimated that 5,000 quantum computers will be operational by 2030** but that the hardware and software necessary for handling the most complex problems won't be available until 2035 or later.


# *Final Exam and Project Info*

- ❑ **Exam held Tue, May 7 • 11:30A - 2:30P • Physics Building 3, Evans 60**
  - ❑ “Comprehensive” Final Exam
  - ❑ Emphasis on second half (~2/3), but some coverage of first half (~1/3)
  - ❑ Same format as Exam 1. Closed-book and notes, one page of notes.
- ❑ Project interviews: Thursday of RRR week, 5/1. Signup!
- ❑ Project final reports due Monday 5/8, midnight.

# *Exam Topics from Second Half*


# How to Design a RISC-V Single-Cycle Processor from the ISA

## Single-Cycle RISC-V RV32I Datapath

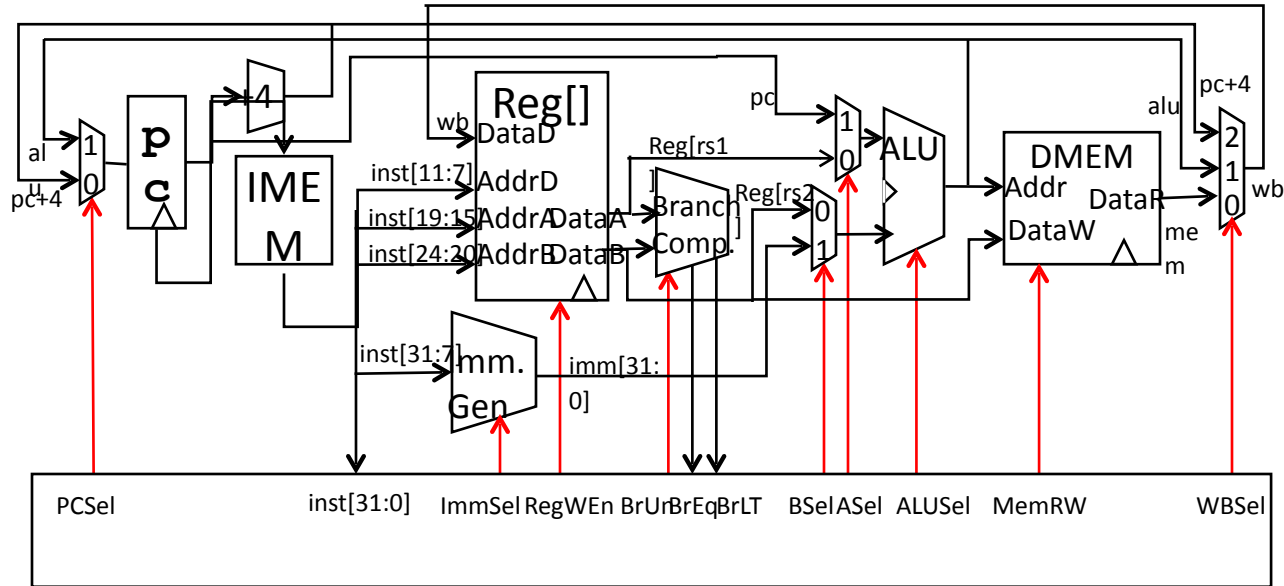

# Processor Pipelining Hazards and Mechanisms


## Pipelined Processor

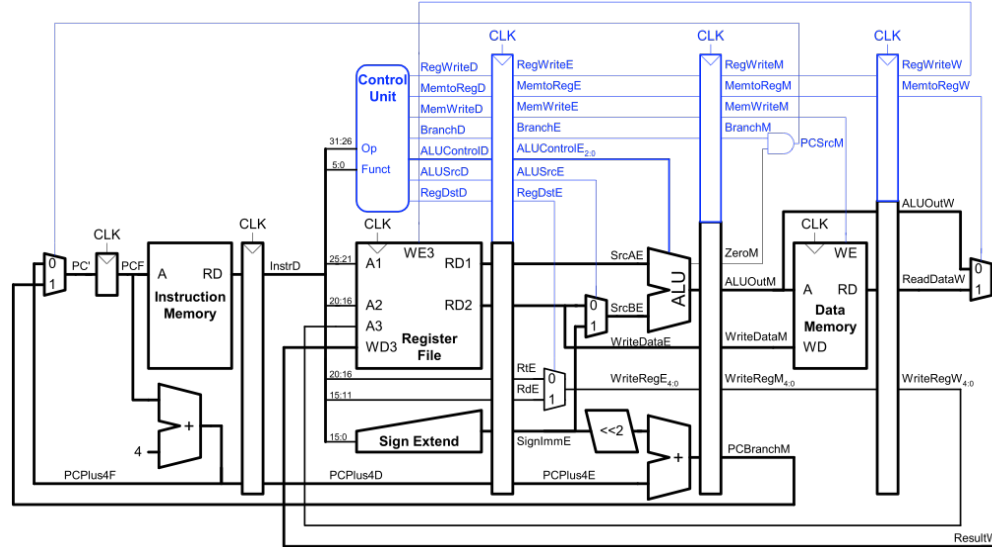


 
# Sources of Power and Energy consumption in Digital ICs

---

Total Power =  $P_{\text{switching}} + P_{\text{short-circuit}} + P_{\text{leakage}}$


  
$$I_{DSub} = k \cdot e^{\frac{-q \cdot V_T}{a \cdot k_a \cdot T}}$$






# Some low-power design techniques

---

- ✱ **Parallelism and pipelining**
- ✱ **Power-down idle transistors**
- ✱ **Slow down non-critical paths**
  
- ✱ **Thermal management**

 *Principles Behind 4 Low-power Design Techniques*



And so, we can transform this:

Vdd

Logic Block →

$P \sim F \times V_{dd}^2$   
 $P \sim 1 \times 1^2$

Freq = 1  
 Vdd = 1  
 Throughput = 1  
 Power = 1  
 Area = 1  
 Pwr Den = 1

Block processes stereo audio. 1/2 of clocks for "left", 1/2 for "right".

Into this:

Top block processes "left", bottom "right".

Vdd/2

Logic Block →

Freq = 0.5  
 Vdd = 0.5  
 Throughput = 1  
 Power = 0.25  
 Area = 2  
 Pwr Den = 0.125

Logic Block →


$P \sim \#blks \times F \times V_{dd}^2$   
 $P \sim 2 \times 1/2 \times 1/4 = 1/4$

CV<sup>2</sup> power only

# Memory Block Internal Architecture

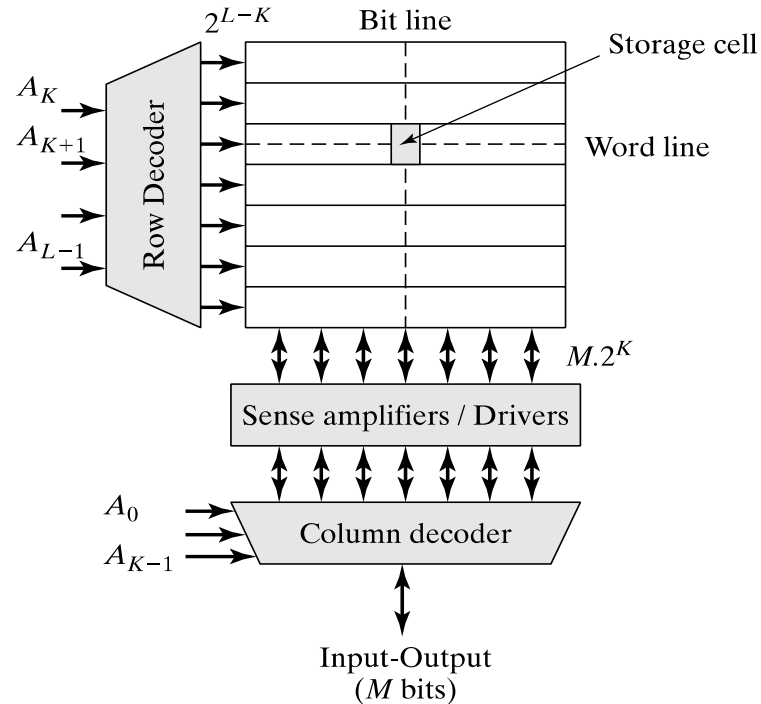
## Memory Architecture Overview

- ❑ **Word lines** used to select a row for reading or writing
- ❑ **Bit lines** carry data to/from periphery
- ❑ **Core aspect ratio** keep close to 1 to help balance delay on word line versus bit line
- ❑ **Address bits** are divided between the two decoders
- ❑ **Row decoder** used to select word line
- ❑ **Column decoder** used to select one or more columns for input/output of data



# SRAM Cell and Read/Write Operation

## SRAM read/write operations

 


## ***Periphery***

- Decoders
- Sense Amplifiers
- Input/Output Buffers
- Control / Timing Circuitry

# Memory Decoder Design
 
## Row Decoder


- Expands L-K address lines into  $2^{L-K}$  word lines



- Example: decoder for 8Kx8 memory block
  - core arranged as 256x256 cells
  - Need 256 AND gates, each driving one word line

# DRAM Cell and Read/Write Operation

## 1-Transistor DRAM Cell

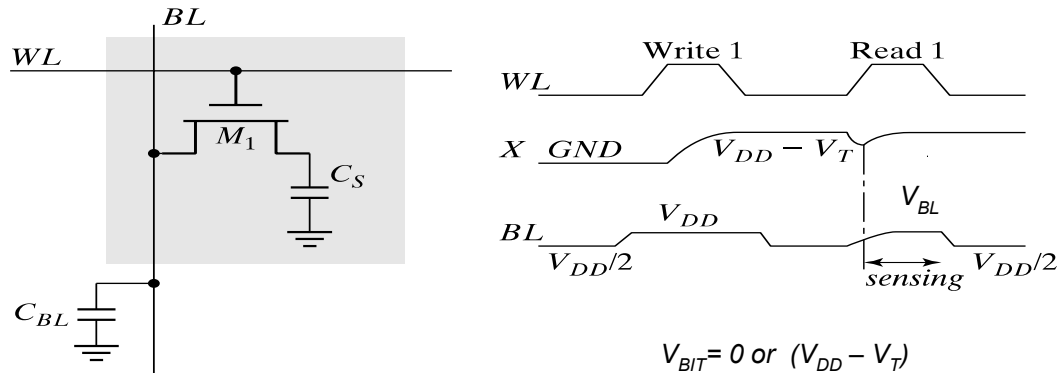


- ❑ To get sufficient  $C_S$ , special IC process is used
- ❑ Cell reading is destructive, therefore read operation always is followed by a write-back
- ❑ Cell loses charge (leaks away in ms - highly temperature dependent), therefore cells occasionally need to be “refreshed” - read/write cycle


# Dual-port Memory Architecture
 
## Dual-ported Memory Internals

- Add decoder, another set of read/write logic, bits lines, word lines:



- Example cell: SRAM

 


- Repeat everything but cross-coupled inverters.
- This scheme extends up to a couple more ports, then need to add additional transistors.


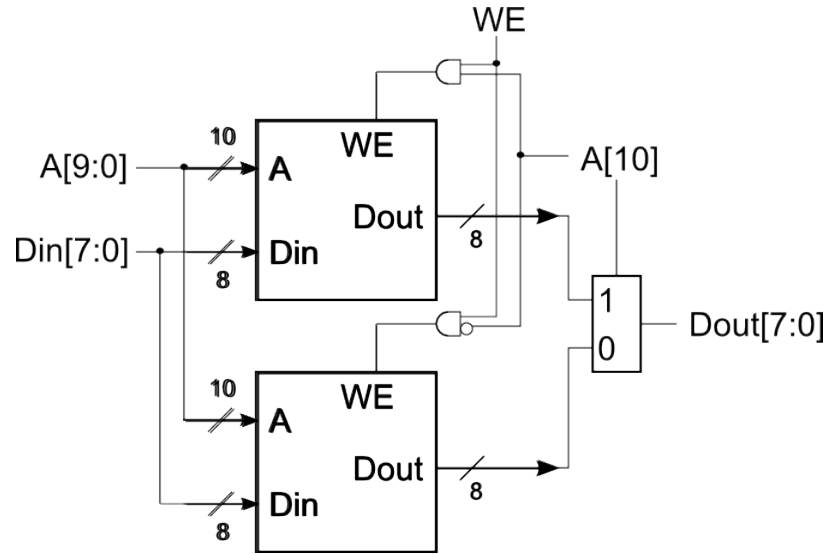
## Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

Increasing the depth. Example: given 1Kx8, want 2Kx8



## FIFO Implementation Details

- Assume, dual-port memory with asynchronous read, synchronous write.
- Binary counter for each of read and write address. CEs (count enable) controlled by WE and RE.
- Equal comparator to see when pointers match.
- State elements for FULL and EMPTY flags:

WE	RE	equal*	EMPTY <sub>i</sub>	FULL <sub>i</sub>
0	0	0	0	0
0	0	1	EMPTY <sub>i-1</sub>	FULL <sub>i-1</sub>
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	EMPTY <sub>i-1</sub>	FULL <sub>i-1</sub>


- Control logic (FSM) with truth-table (draft) shown to left.

\* Actually need 2 signals: “will be equal after read” and “will be equal after write”


# Serialization versus Parallelization in Iterative Computations
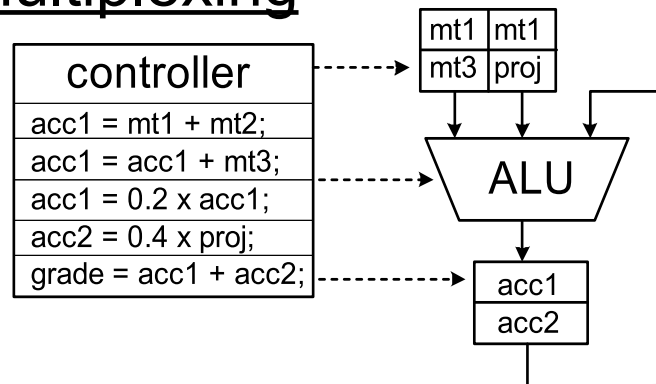
## Time-Multiplexing


- *Time multiplex* single ALU for all adds and multiplies:
- Attempts to minimize cost at the expense of time.
  - Need to add extra register, muxes, control.



 - If we adopt above approach, we can then consider the combinational hardware circuit diagram as an *abstract computation-graph*.



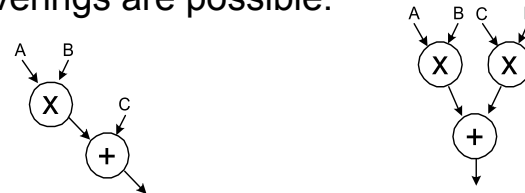Using other primitives, other coverings are possible.




- This time-multiplexing “covers” the computation graph by performing the action of each node one at a time. (Sort of *emulates* it.)

# Principles of Pipelining and Restrictions of Loops
 
## Limits on Pipelining

- Without FF overhead, throughput improvement  $\propto$  # of stages.
- After many stages are added FF overhead begins to dominate:



- Other limiters to effective pipelining: # of stages
  - clock skew contributes to clock overhead
  - unequal stages
  - FFs dominate cost
  - clock distribution power consumption
  - [feedback \(dependencies between loop iterations\)](#)

# Principles of Pipelining and Restrictions of Loops




## Pipelining Loops with Feedback

“Loop carry dependency”

However, we can overlap the “non-feedback” part of the iterations:

Add is associative and commutative. Therefore we can reorder the computation to shorten the delay of the feedback path:
   
$$y_i = (y_{i-1} + x_i) + a = (a + x_i) + y_{i-1}$$




“Shorten” the feedback path.

- Pipelining is limited to 2 stages.

# List Processor Design and Optimizations

## 5. Optimization, Architecture #4

### □ Datapath:

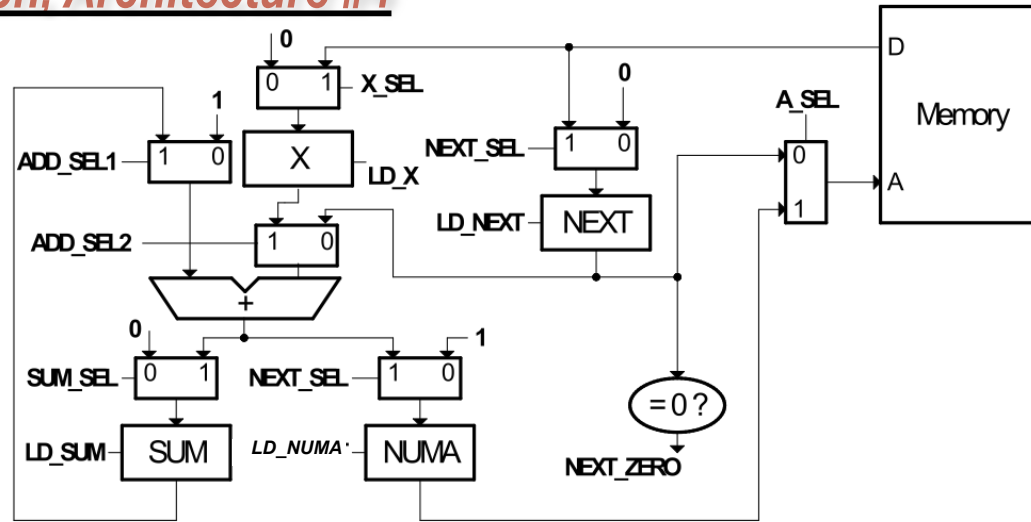

### □ Incremental cost:

- Addition of another register & mux, adder mux, and control.


### □ Performance: find max time of the four actions

1.  $X \leftarrow \text{Memory}[\text{NUMA}]$ ,  $0.5 + 1 + 10 + 1 + 0.5 = 13\text{ns}$   
 $\text{NUMA} \leftarrow \text{NEXT} + 1$ ; same for all  $\Rightarrow T > 13\text{ns}, F < 77\text{MHz}$
2.  $\text{NEXT} \leftarrow \text{Memory}[\text{NEXT}]$ ,  
 $\text{SUM} \leftarrow \text{SUM} + X$ ;

# Carry Select Adder Design
 
## Carry Select Adder

- Extending Carry-select to multiple blocks





- What is the optimal # of blocks and # of bits/block?
  - If blocks too small delay dominated by total mux delay
  - If blocks too large delay dominated by adder ripple delay

$\sqrt{N}$  stages of  $\sqrt{N}$  bits

$T \propto \text{sqrt}(N)$ ,  
 $\text{Cost} \approx 2 * \text{ripple} + \text{muxes}$

# Carry Lookahead and Parallel Prefix Adders

## Parallel Prefix Adder Example

  


$$\begin{aligned}
 G &= g_3 + g_2 p_3 + (g_1 + g_0 p_1) p_3 p_2 \\
 &= g_3 + g_2 p_3 + g_1 p_3 p_2 + g_0 p_3 p_2 p_1 \\
 &= c_4
 \end{aligned}$$

$$s_i = a_i \oplus b_i \oplus c_i = p_i \oplus c_i$$



# Bit-serial Adder

## Bit-Serial Addition

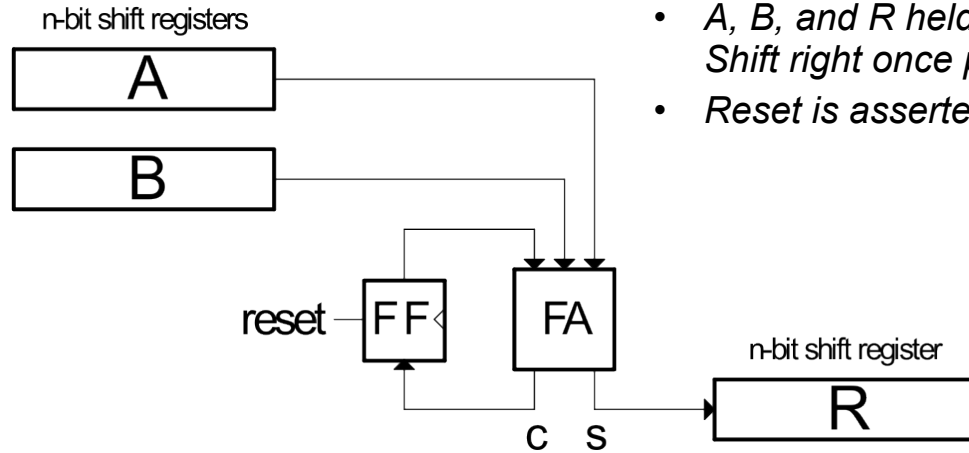


- *A, B, and R held in shift-registers. Shift right once per clock cycle.*
- *Reset is asserted by controller.*

### □ Addition of 2 n-bit numbers:

- takes n clock cycles,
- uses 1 FF, 1 FA cell, plus registers
- the bit streams may come from or go to other circuits, therefore the registers might not be needed.

# Array Multiplier Design


## Combinational Multiplier (unsigned)

 

— multiplicand  
— multiplier

Partial products, one for each bit in multiplier (each bit needs just one AND gate)

Propagation delay  $\sim 2N$

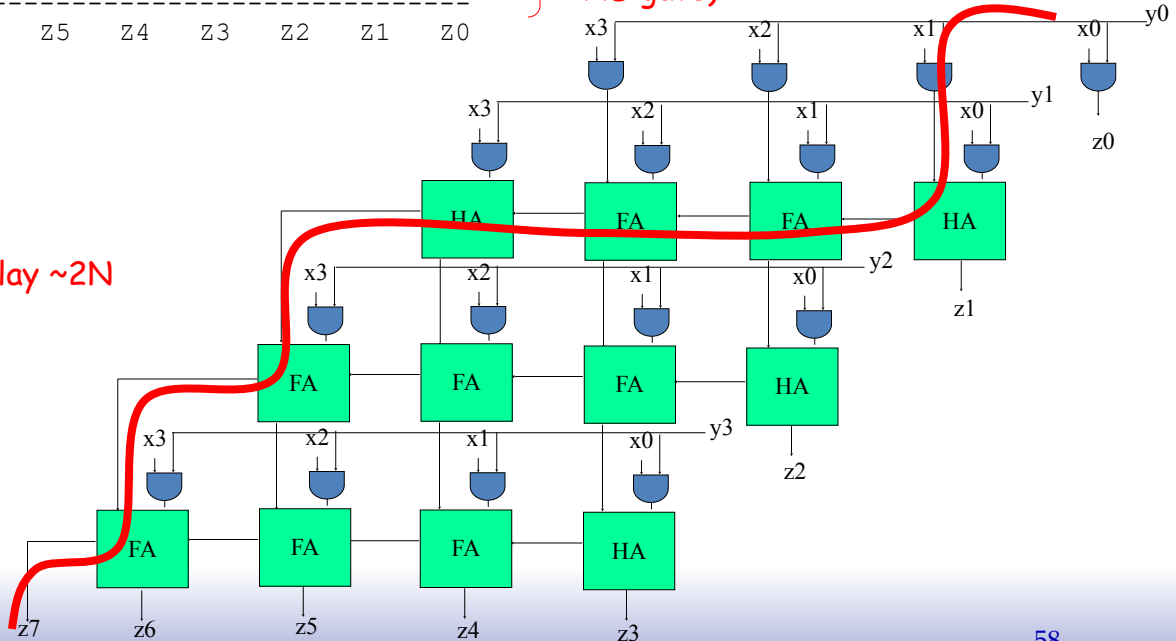

# Carry-Save Addition

- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.


- Example: sum three numbers,  $3_{10} = 0011$ ,  $2_{10} = 0010$ ,  $3_{10} = 0011$

	$3_{10}$	0011	
	+	$2_{10}$	0010
		<hr style="width: 100%;"/>	
		c 0100 = $4_{10}$	}
		s 0001 = $1_{10}$	
carry-save add	}		
	$3_{10}$	0011	
		<hr style="width: 100%;"/>	
		c 0010 = $2_{10}$	}
		s 0110 = $6_{10}$	
carry-propagate add	}	<hr style="width: 100%;"/>	
		1000 = $8_{10}$	

- In general, *carry-save* addition takes in 3 numbers and produces 2.
  - Sometimes called a “3:2 compressor”: 3 input signals into 2 in a potentially lossy operation
- Whereas, *carry-propagate* takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition

# Signed Multiplication

## 2's Complement Multiplication

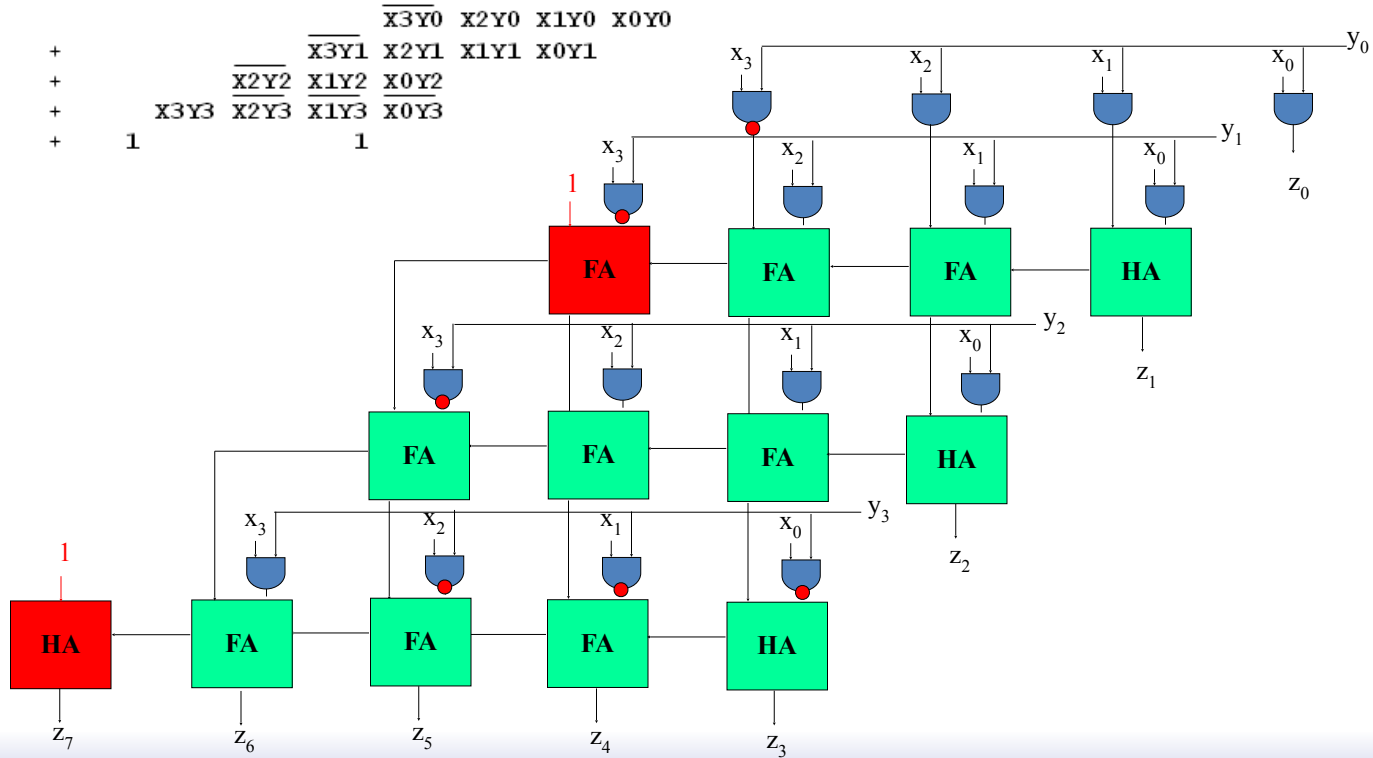

# CSD Multiplier Design

## Canonical Signed Digit Representation

- CSD represents numbers using 1,  $\bar{1}$ , & 0 with the least possible number of non-zero digits.
  - Strings of 2 or more non-zero digits are replaced.
  - Leads to a unique representation.

- To form CSD representation might take 2 passes:

- First pass: replace all occurrences of 2 or more 1's:

$01..10$  by  $10..1\bar{0}$

- Second pass: same as above, plus replace  $0110$  by  $0010$  and  $011\bar{0}$  by  $001\bar{0}$  —

- Examples:


	$0010111 = 23$	$0110110 = 54$
$011101 = 29$	$001100\bar{1}$	$10\bar{1}10\bar{1}0$
$100\bar{1}01 = 32 - 4 + 1$	$010\bar{1}00\bar{1} = 32 - 8 - 1$	$100\bar{1}0\bar{1}0 = 64 - 8 - 2$

- Can we further simplify the multiplier circuits?

# Log and Barrel Shifters Design and Analysis

 
## Log Shifter / Rotator

- Log(N) stages, each shifts (or not) by a power of 2 places,  $S=[s_2;s_1;s_0]$ :


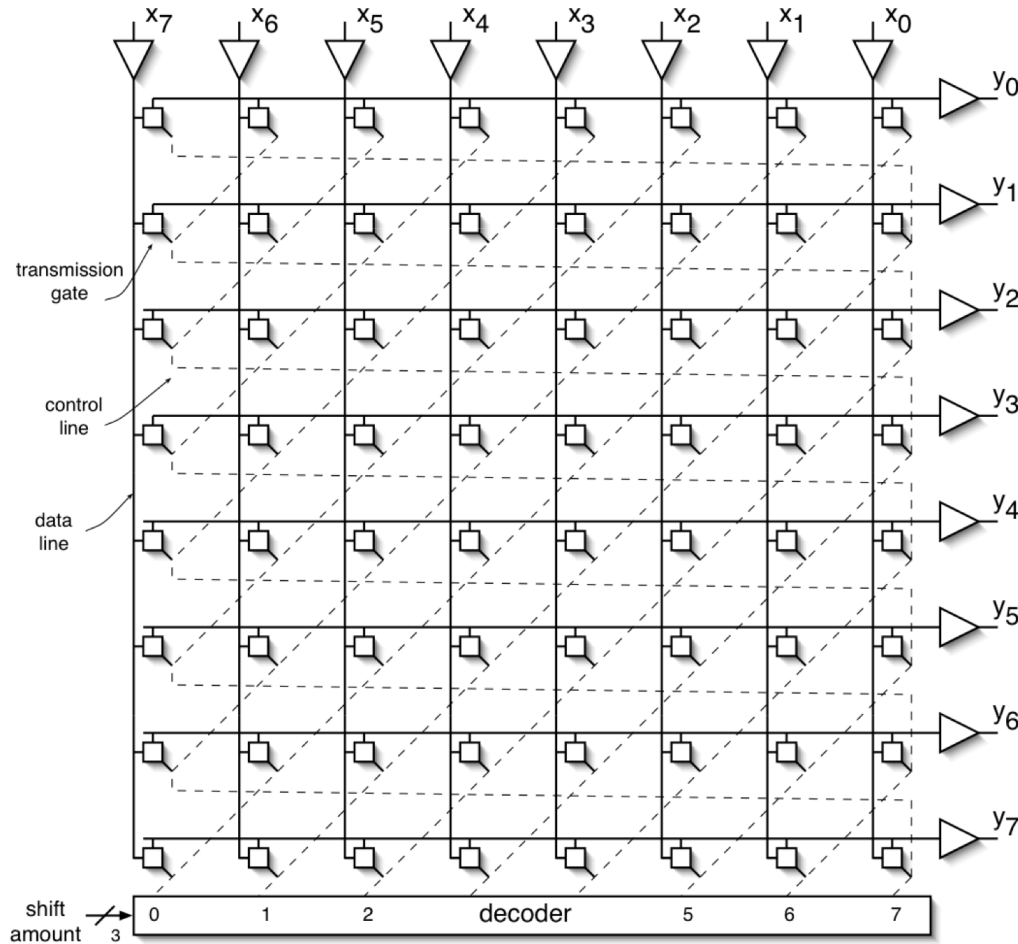
# Barrel Shifter

Log and Barrel Shifters Design and Analysis



Cost/delay?

- (don't forget the decoder)

## **Clock Constraints in Edge-Triggered Systems**

If launching edge is late and receiving edge is early, the data will not be too late if:

$$t_{clk-q,max} + t_{logic,max} + t_{setup} < T_{CLK} - t_{JS,1} - t_{JS,2} + \delta$$

Minimum cycle time is determined by the maximum delays through the logic

$$t_{clk-q,max} + t_{logic,max} + t_{setup} - \delta + 2t_{JS} < T_{CLK}$$

**Skew can be either positive or negative**

**Jitter  $t_{JS}$  usually expressed as peak-to-peak or  $n \times$  RMS value**



# Clock Constraints in Edge-Triggered Systems

If launching edge is early and receiving edge is late:

$$t_{clk-q,min} + t_{logic,min} - t_{JS,1} > t_{hold} + t_{JS,2} + \delta$$

Minimum logic delay


$$t_{clk-q,min} + t_{logic,min} > t_{hold} + 2t_{JS} + \delta$$

(This assumes jitter at launching and receiving clocks are independent – which usually is not true)

# Source of Clock Uncertainties



## Clock Uncertainties

### Sources of clock uncertainty

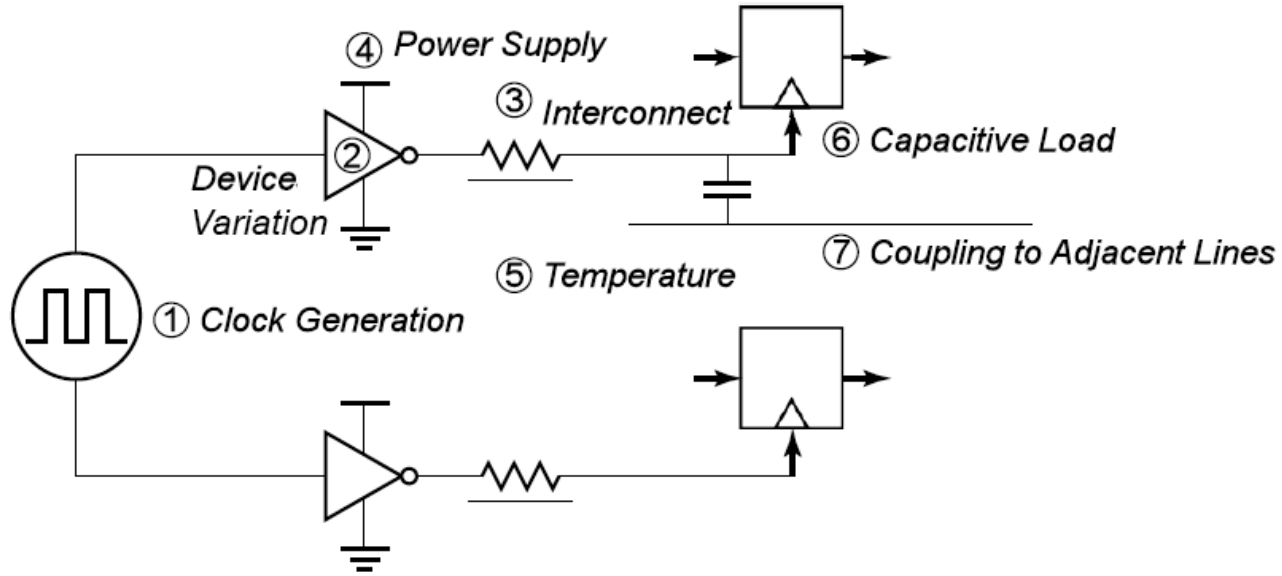

# H-Tree

## Principles of Good Clock Distribution

 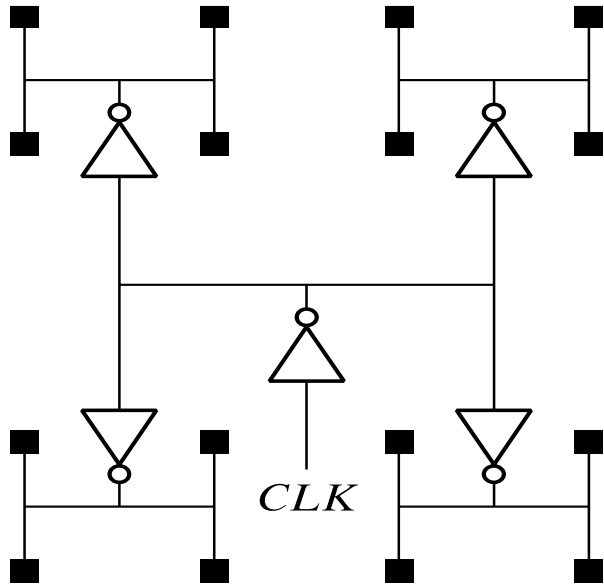

Equal wire length/number of buffers to get to every location



**TA: Kevin Anderson**  
Discussion, ASIC Lab,  
PS, Ed, OH: TBA



**TA: Justin Kalloor**  
Discussion, PS,  
OH: TBA



**UCS2: Kevin He**  
Discussion, ASIC Lab,  
web, OH: TBA




**UCS2: Daniel Endraws**  
FPGA Labs, OH: TBA



**UCS2: Dhruv Vaish**  
FPGA Lab, Discussion,  
OH: TBA



**UCS2: Rohit Kanagal**  
FPGA Lab, OH: TBA

 

**UCS1: Allen Chen**  
PS grading, Discussion,  
OH: TBA



**UCS1: Reuben Thomas**  
PS grading, OH: TBA

# *The End.*

- ❑ Special thanks to our TAs, UCS1s, UCS2s, ...
- ❑ Good luck finishing up your project and on the final!
- ❑ Thanks for a great semester!