


EECS 151/251A

Spring 2024

**Digital Design and Integrated
Circuits**

Instructor: Wawrzynek

 **Lecture 3: Verilog 1:
Combinational Logic Circuits**




Outline

Hardware Description
Language Overview

Verilog Introduction

Announcements

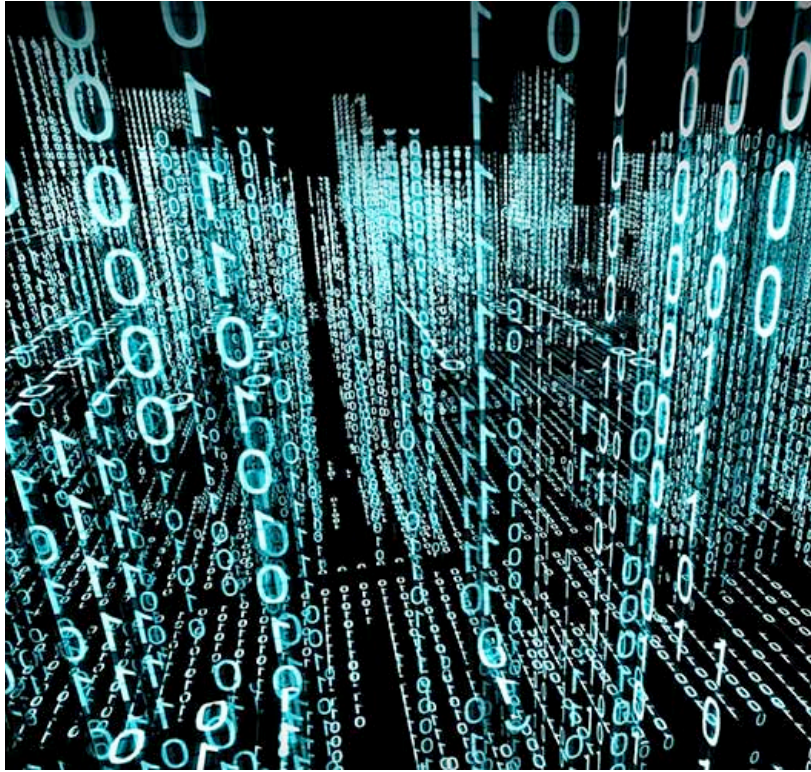
- ❑ Problem Set one posted. Start soon!
 - ❑ Due next Monday (another out Friday)
- ❑ Contact me if you are still trying to get enrolled.



Hardware Description Languages

Design Entry

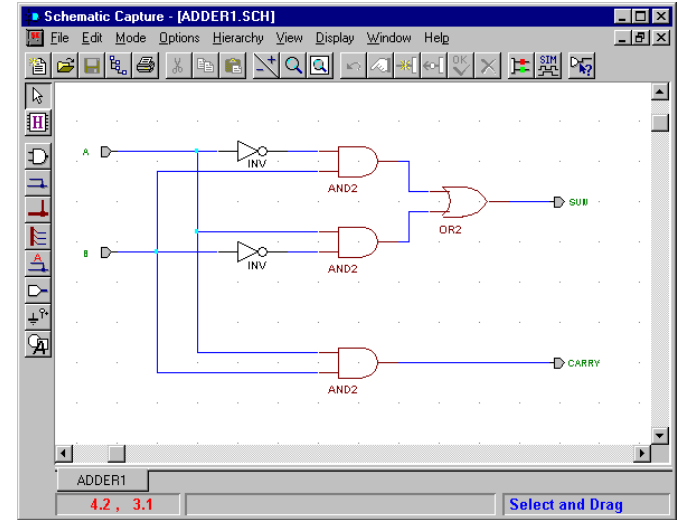- ❑ Schematic entry/editing used to be the standard method in industry and universities.
- ☺ Schematics are intuitive. They match our use of gate-level or block diagrams.
- ☺ Somewhat physical. They imply a physical implementation.
- ☹ Require a special tool (editor).
- ☹ Unless hierarchy is carefully designed, schematics can be confusing and difficult to follow on large designs.



- Hardware Description Languages (HDLs) are the new standard
 - except for PC board design, where schematics are still used.

Hardware Description Languages

- Basic Idea:
 - Language constructs describe circuits with two basic forms:
 - **Structural descriptions:** connections of components. Nearly one-to-one correspondence to with schematic diagram.
 - **Behavioral descriptions:** use high-level constructs (similar to conventional programming) to describe the circuit function.
- Originally invented for simulation.
 - “logic synthesis” tools exist to automatically convert to gate level representation.
 - High-level constructs greatly improves designer productivity.
 - However, this may lead you to falsely believe that hardware design can be reduced to writing programs*

“Structural” example:

```
Decoder(output x0,x1,x2,x3;  
inputs a,b)  
{  
    wire abar, bbar;  
    inv(bbar, b);  
    inv(abar, a);  
    and(x0, abar, bbar);  
    and(x1, abar, b );  
    and(x2, a, bbar);  
    and(x3, a, b );  
}
```

“Behavioral” example:


```
Decoder(output x0,x1,x2,x3;  
inputs a,b)  
{  
    switch [a b]  
        case 00: [x0 x1 x2 x3] = 0x8;  
        case 01: [x0 x1 x2 x3] = 0x4;  
        case 10: [x0 x1 x2 x3] = 0x2;  
        case 11: [x0 x1 x2 x3] = 0x1;  
    endswitch;  
}
```

Warning: this is a fake HDL!

*New tools and languages exist for this - called “high level synthesis”.

Sample Design Methodology

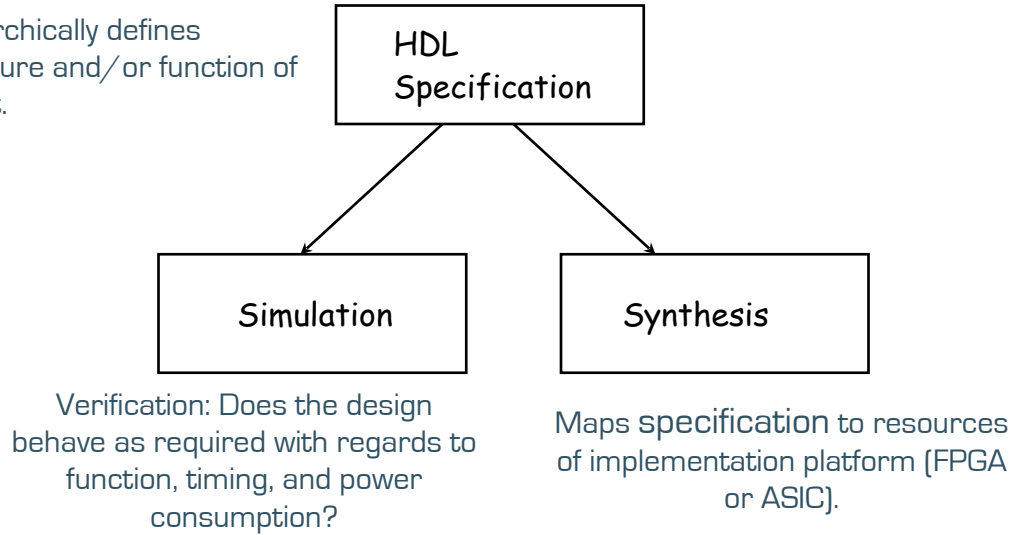Hierarchically defines structure and/or function of circuit.



Note: This is not the entire story. Other tools are useful for analyzing HDL specifications. More on this later.

Some Hardware Description Languages

Verilog:

- Simple C-like syntax for structural and behavior hardware constructs
- Mature set of commercial tools for synthesis and simulation
- Used in EECS 151 / 251A

VHDL:

- Semantically very close to Verilog
- More syntactic overhead
- Extensive type system for “synthesis time” checking

System Verilog:


- Enhances Verilog with strong typing along with other additions
- Somewhat less mature tool-flow

BlueSpec:

- Invented at MIT
- Originally built within the Haskell programming language
- Now available commercially: bluespec.com

Chisel:

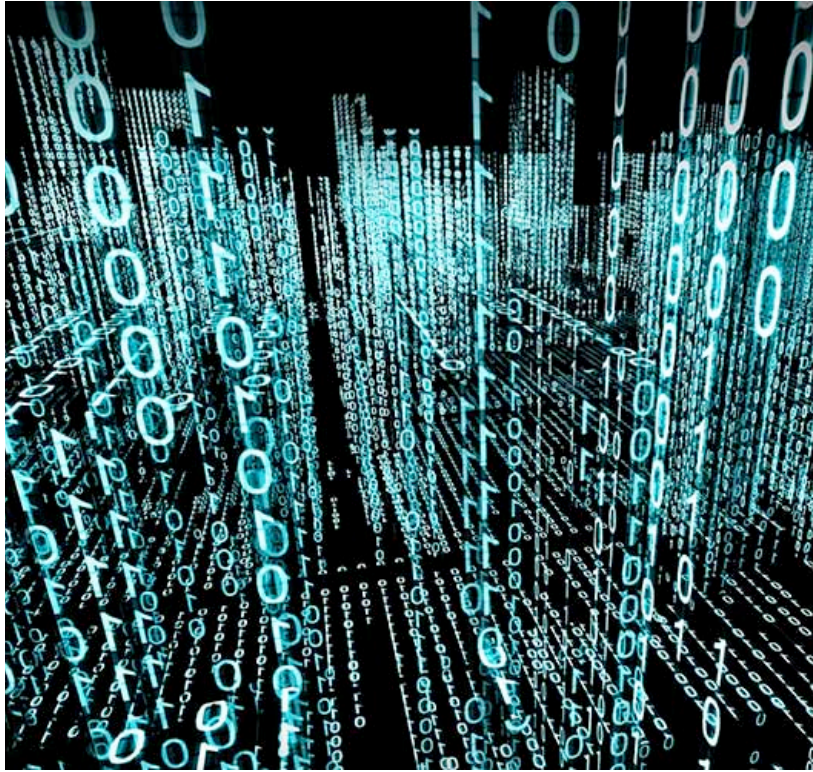- Developed at UC Berkeley
- Used in CS152, and research projects
- Available at: www.chisel-lang.org




Verilog Introduction

Verilog Introduction

- ❑ A module definition describes a component in a circuit
- ❑ Two ways to describe module contents:
 - Structural Verilog
 - List of sub-components and how they are connected
 - Just like schematics, but using text
 - You get precise control over circuit details
 - May be necessary to map to special resources of the FPGA/ASIC
 - Behavioral Verilog
 - Describe what a component does, not how it does it
 - May be simpler to write than structural description
 - Synthesized into a circuit that has this behavior
 - Result is only as good as the tools
- ❑ Build up a hierarchy of modules. Top-level module is your entire design (or the environment to test your design).
- ❑ *Common approach is to use behavioral descriptions for “leaf cells” and structural to build hierarchy.*

Verilog Modules and Instantiation

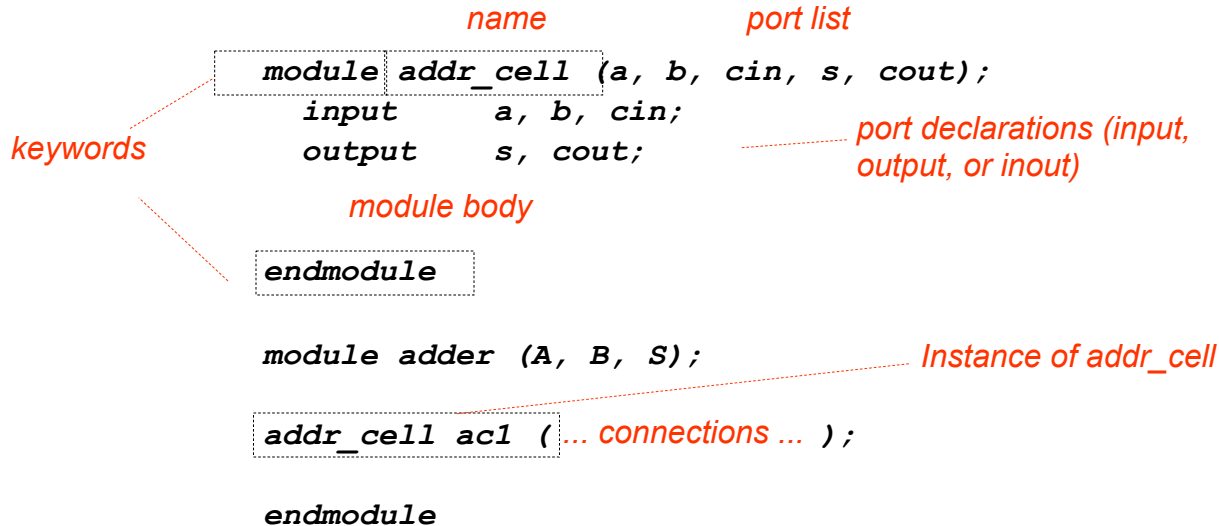- ❑ Modules define circuit components.
- ❑ Instantiation defines hierarchy of the design.



Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.

Note: Verilog syntax allows port declarations in port list.

Structural Model - XOR example

```
module xor_gate ( out, a, b );
```

module name

```
  input  a, b;
```

port list

```
  output out;
```

port declarations

```
  wire  aBar, bBar, t1, t2;
```

internal signal declarations

Built-in gates

```
  not invA (aBar, a);
```


instances

```
  not invB (bBar, b);
```

```
  and and1 (t1, a, bBar);
```

```
  and and2 (t2, b, aBar);
```

```
  or or1 (out, t1, t2);
```

 

```
endmodule
```


Interconnections (note output is first)

Instance name


■ Notes:

- The instantiated gates are not “executed”. They are active always.
- xor gate already exists as a built-in (so really no need to define it).

Structural Example: 2-to1 mux

 

a) 2-input mux symbol

 

b) 2-input mux gate-level circuit diagram

```
/* 2-input multiplexor in gates */  
module mux2 (in0, in1, select, out);  
    input in0,in1,select;  
    output out;  
    wire s0,w0,w1;  
  
    not (s0, select);  
    and (w0, s0, in0),  
        (w1, select, in1);  
    or (out, w0, w1);  
  
endmodule // mux2
```


**Built-ins don't need
Instance names**

**C++ style
comments**


**Multiple instances can
share the same
"master" name.**

**Built-ins gates can
have > 2 inputs. Ex:
and (w0, a, b, c, d);**

Instantiation, Signal Array, Named ports

 

a) 4-input mux symbol

 

b) 4-input mux implemented with 2-input muxes

```
*/ 2-input multiplexor in gates */  
odule mux2 (in0, in1, select, out);  
  input in0,in1,select;  
  output out;  
  wire s0,w0,w1;  
  not (s0, select);  
  and (w0, s0, in0),  
      (w1, select, in1);  
  or (out, w0, w1);  
ndmodule // mux2
```

```
module mux4 (in0, in1, in2, in3, select, out);
```

```
  input in0,in1,in2,in3;
```

```
  input [1:0] select;
```

Signal array. Declares select[1], select[0]

```
  output out;
```

```
  wire w0,w1;
```

Named ports. Highly recommended.

```
    mux2
```

```
      m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
```

```
      m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
```

```
      m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
```

```
endmodule // mux4
```


Simple Behavioral Model

```
module foo (out, in1, in2);  
  input      in1, in2;  
  output     out;
```

```
  assign out = in1 & in2;
```

```
endmodule
```

“continuous assignment”


Connects out to be the “and” of in1 and in2.

The assignment continuously happens, therefore any change on the rhs is reflected in out immediately (except for the small delay associated with the implementation of the &).


Not like an assignment in C that takes place when the program counter gets to that place in the program.

Example - Ripple Adder

```
module FullAdder(a, b, ci, r, co);  
    input a, b, ci;  
    output r, co;  
  
    assign r = a ^ b ^ ci;  
    assign co = a&ci | a&b | b&ci;  
  
endmodule
```

 

```
module Adder(A, B, R);  
    input [3:0] A;  
    input [3:0] B;  
    output [4:0] R;  
  
    wire c1, c2, c3;  
  
    FullAdder  
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
  
endmodule
```

 

Verilog Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{{}}	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

Verilog Numbers

Constants:

14 ordinary decimal number

-14 2's complement representation

12'b0000_0100_0110 binary number (“_” is ignored)

12'h046 hexadecimal number with 12 bits

Signal Values:

By default, Values are unsigned

e.g., $C[4:0] = A[3:0] + B[3:0];$


if $A = 0110$ (6) and $B = 1010$ (treated as 10 not -6)

$C = 10000$ not 00000

i.e., B is zero-padded, not sign-extended

wire signed [31:0] x;

 Declares a signed (2's complement) signal array.



Verilog Assignment Types

Continuous Assignment Examples

```
wire [3:0] A, X, Y, R, Z;  
wire [7:0] P;  
wire r, a, cout, cin;
```

```
assign R = X | (Y & ~Z);
```

```
assign r = &X;
```

example
reduction
operator

use of bit-wise Boolean operators

```
assign R = (a == 1'b0) ? X : Y;
```

conditional operator

```
assign P = 8'hff;
```

example constants

```
assign P = X * Y;
```

arithmetic operators (use with care!)

```
assign P[7:0] = {4{X[3]}, X[3:0]};
```

(ex: sign-extension)

```
assign {cout, R} = X + Y + cin;
```

bit field concatenation

```
assign Y = A << 2;
```

bit shift operator

```
assign Y = {A[1], A[0], 1'b0, 1'b0};
```

equivalent bit shift

Non-continuous Assignments

A bit strange from a hardware specification point of view. Shows off Verilog roots as a simulation language.

“always” block example:

```
module and_or_gate (out, in1, in2, in3);
```

```
  input      in1, in2, in3;
```

```
  output    out;
```

```
  reg      out;
```

“reg” type declaration, needed for always block assignment. Not really a register in this case. Just a Verilog idiosyncrasy.

```
  always @(in1 or in2 or in3) begin
```

```
    out = (in1 & in2) | in3;
```

```
  end
```

“sensitivity” list, triggers the action in the body.

keyword

```
endmodule
```

brackets multiple statements (not necessary in this example).

Isn't this just: `assign out = (in1 & in2) | in3;?`

Why bother?

Always Blocks

Always blocks give us some constructs that are impossible or awkward in continuous assignments.

case statement example:

```
module mux4 (in0, in1, in2, in3, select, out);  
  input in0,in1,in2,in3;  
  input [1:0] select;  
  output      out;  
  reg         out;
```

```
  always @ (in0 in1 in2 in3 select)
```

```
    case (select)
```

```
      2'b00: out=in0;
```

```
      2'b01: out=in1;
```

```
      2'b10: out=in2;
```

```
      2'b11: out=in3;
```

```
    endcase
```

```
  endmodule // mux4
```

keyword

The statement(s) corresponding to whichever constant matches "select", get applied.

Couldn't we just do this with nested "if"s?

Well yes and no!

Always Blocks

Nested if-else example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output      out;
  reg        out;


  always @ (in0 in1 in2 in3 select)
    if (select == 2'b00) out=in0;
    else if (select == 2'b01) out=in1;
    else if (select == 2'b10) out=in2;
    else out=in3;
endmodule // mux4
```

Nested if structure leads to “priority logic” structure, with different delays for different inputs (in3 to out delay > than in0 to out delay). Case version treats all inputs the same.

Defining Processor ALU in 5 mins

- Modularity is essential to the success of large designs
- High-level primitives enable direct synthesis of behavioral descriptions (functions such as additions, subtractions, shifts (<< and >>), etc.

Example: A 32-bit ALU

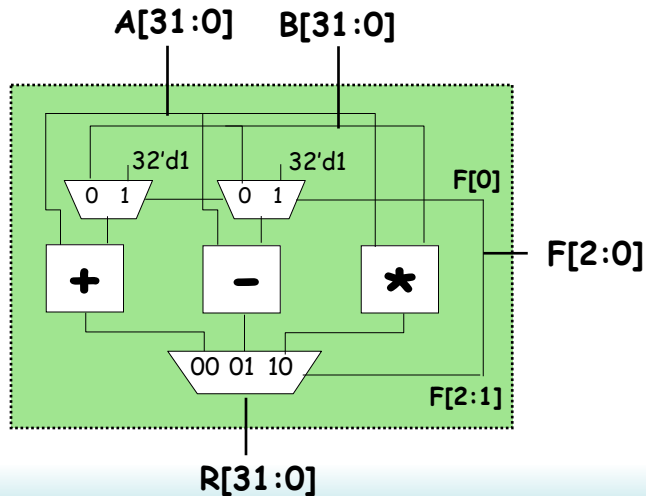

Function Table

F2	F1	F0	Function
0	0	0	$A + B$
0	0	1	$A + 1$
0	1	0	$A - B$
0	1	1	$A - 1$
1	0	X	$A * B$

Module Definitions

2-to-1 MUX

```
module mux32two(i0,i1,sel,out);  
input [31:0] i0,i1;  
input sel;  
output [31:0] out;  
  
assign out = sel ? i1 : i0;  
  
endmodule
```

3-to-1 MUX

```
module mux32three(i0,i1,i2,sel,out);  
input [31:0] i0,i1,i2;  
input [1:0] sel;  
output [31:0] out;  
reg [31:0] out;  
  
always @ (i0 or i1 or i2 or sel)  
begin  
    case (sel)  
        2'b00: out = i0;  
        2'b01: out = i1;  
        2'b10: out = i2;  
        default: out = 32'bx;  
    endcase  
end  
endmodule
```

32-bit Subtractor

```
module sub32(i0,i1,diff);  
input [31:0] i0,i1;  
output [31:0] diff;  
  
assign diff = i0 - i1;  
  
endmodule
```

32-bit Adder

```
module add32(i0,i1,sum);  
input [31:0] i0,i1;  
output [31:0] sum;  
  
assign sum = i0 + i1;  
  
endmodule
```

16-bit Multiplier

```
module mul16(i0,i1,prod);  
input [15:0] i0,i1;  
output [31:0] prod;  
  
// this is a magnitude multiplier  
// signed arithmetic later  
assign prod = i0 * i1;  
  
endmodule
```


Top-Level ALU Declaration

- Given submodules:

```
module mux32two(i0,i1,sel,out);  
module mux32three(i0,i1,i2,sel,out);  
module add32(i0,i1,sum);  
module sub32(i0,i1,diff);  
module mul16(i0,i1,prod);
```

- Declaration of the ALU Module:


```
module alu(a, b, f, r);  
  input [31:0] a, b;  
  input [2:0] f;  
  output [31:0] r;  
  
  wire [31:0] addmux_out, submux_out;  
  wire [31:0] add_out, sub_out, mul_out;  
  
  mux32two  adder_mux(.io(b), .i1(32'd1), .sel(f[0]), .out(addmux_out));  
  mux32two  sub_mux(.io(b), .i1(32'd1), .sel(f[0]), .out(submux_out));  
  add32     our_adder(.i0(a), .i1(addmux_out), .sum(add_out));  
  sub32     our_subtractor(.i0(a), .i1(submux_out), .diff(sub_out));  
  mul16     our_multiplier(.i0(a[15:0]), .i1(b[15:0]), .prod(mul_out));  
  mux32three output_mux(.i0(add_out), .i1(sub_out), .i2(mul_out), .sel(f[2:1]), .out(r));  
endmodule
```

 

Top-Level ALU Declaration, take 2

- ❑ No Hierarchy:
- ❑ Declaration of the ALU Module:

 
```
module alu(a, b, f, r);  
  input [31:0] a, b;  
  input [2:0] f;  
  output [31:0] r;  
  always @ (a or b or f)  
    case (f)  
      3'b000: r = a + b;  
      3'b001: r = a + 1'b1;  
      3'b010: r = a - b;  
      3'b011: r = a - 1'b1;  
      3'b100: r = a * b;  
      default: r = 32'bx;  
    endcase  
endmodule
```




Will this synthesize into 2 adders and 2 subtractors or 1 of each?

Review - Ripple Adder Example
 
```
module FullAdder(a, b, ci, r, co);  
  input a, b, ci;  
  output r, co;  
  
  assign r = a ^ b ^ ci;  
  assign co = a&ci + a&b + b&cin;  
  
endmodule
```


 
```
module Adder(A, B, R);  
  input [3:0] A;  
  input [3:0] B;  
  output [4:0] R;  
  
  wire c1, c2, c3;  
  FullAdder  
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
  
endmodule
```



Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

```
module Adder(A, B, R);  
  parameter N = 4;  
  input [N-1:0] A;  
  input [N-1:0] B;  
  output [N:0] R;  
  wire [N:0] C;
```

Declare a parameter with default value.

Note: this is not a port. Acts like a “synthesis-time” constant.

Replace all occurrences of “4” with “N”.

variable exists only in the specification - not in the final circuit.

```
  genvar i;
```

Keyword that denotes synthesis-time operations

```
  generate
```

For-loop creates instances (with unique names)

```
    for (i=0; i<N; i=i+1) begin:bit
```

```
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));
```

```
    end
```

```
  endgenerate
```

```
  assign C[0] = 1'b0;
```

```
  assign R[N] = C[N];
```

```
endmodule
```

```
Adder adder4 ( ... );
```

```
Adder #(.N(64))
```

```
adder64 ( ... );
```

**Overwrite parameter
N at instantiation.**

More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
module gray2bin1 (bin, gray);
    parameter SIZE = 8;
    output [SIZE-1:0] bin;
    input  [SIZE-1:0] gray;

    genvar i;

    generate for (i=0; i<SIZE; i=i+1) begin:bit
        assign bin[i] = ^gray[SIZE-1-i];
    end:bit
endgenerate
endmodule
```

variable exists only in the specification - not in the final circuit.

Keywords that denotes synthesis-time operations

For-loop creates instances of assignments

Loop must have constant bounds

generate if-else-if based on an expression that is deterministic at the time the design is synthesized.

generate case : selecting case expression must be deterministic at the time the design is synthesized.

Verilog in EECS 151/251A

- ❑ We use behavioral modeling at the bottom of the hierarchy
- ❑ Use instantiation to 1) build hierarchy and, 2) map to FPGA and ASIC resources not supported by synthesis.
- ❑ Favor continuous assign and avoid always blocks unless:
 - no other alternative: ex: state elements, case
 - helps readability and clarity of code: ex: large nested if else
- ❑ Use named ports.
- ❑ Verilog is a big language. This is only an introduction.
 - Complete IEEE Verilog-Standard document (1364-2005) linked to class website.
 - Harris & Harris book chapter 4 is a good source.
 - **Be careful of what you read on the web.** Many bad examples out there.
 - We will be introducing more useful constructs throughout the semester. Stay tuned!