

**EECS 151/251A**

**Spring 2024**

**Digital Design and Integrated  
Circuits**

Instructor:


John Wawrzynek

Lecture 6:

Combinational Logic  
Representations

 
# *Announcements*

- ❑ **PS 2 due tonight!**
- ❑ HW 3 posted, due in a week.



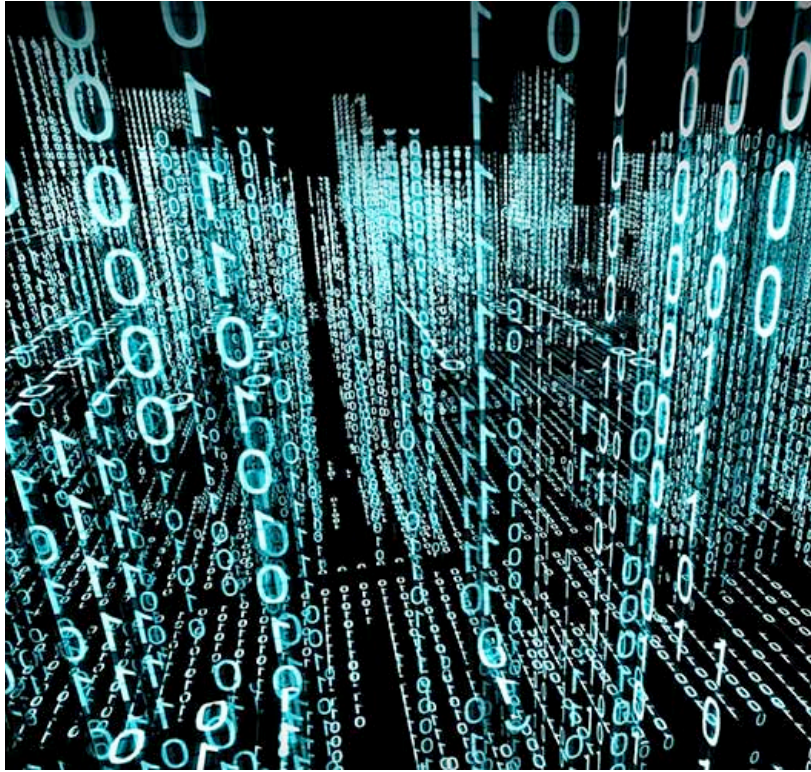
# Outline

- *Three representations for combinational logic:*
  - *truth tables,*
  - *graphical (logic gates), and*
  - *algebraic equations*
- *Boolean Algebra*
- *Boolean Simplification*
- *Multi-level Logic,*
- *NAND/NOR*
- *XOR*



# Representations of Combinational Logic

# Combinational Logic (CL) Defined

 


$y_i = f_i(x_0, \dots, x_{n-1})$ , where  $x, y$  take on values  $\{0,1\}$ .

$Y$  is a function of only  $X$ , i.e., it is a “pure function”.

- If we change  $X$  then  $Y$  will change immediately (well almost!).
  - There is an **implementation dependent** delay from  $X$  to  $Y$ .
  - $Y$  is a function of nothing other than the current inputs values.

# CL Block Example #1

 

Truth Table Description:


$x_0$	$x_1$	$y$
0	0	0
0	1	1
1	0	1
1	1	0

Boolean Equation:

$$y_0 = [x_0 \text{ AND } \text{not}(x_1)] \\ \text{OR } [\text{not}(x_0) \text{ AND } x_1]$$

$$y_0 = x_0x_1' + x_0'x_1$$

Gate Representation:

 

# Boolean Algebra/Logic Circuits

## ❑ Why are they called “logic circuits”?

- ❑ Logic: The study of the principles of reasoning.
- ❑ The 19th Century Mathematician, George Boole, developed a math. system (algebra) involving logic, Boolean Algebra.
- ❑ His variables took on TRUE, FALSE
- ❑ Later Claude Shannon (father of information theory) showed (in his Master's thesis!) how to map Boolean Algebra to digital circuits:



## ❑ Primitive functions of Boolean Algebra:

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

*Why was this novel/innovative?*




# Other logic functions of 2 variables (x,y)

xy	f0	f1													
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0

↙
↙
↙
↙
↙
↙
↙
↙
↙
↙
↙
↙
↙
↙
↙
↙



0   AND   X   Y ⊕   OR   NOR   XNOR   NAND   1

Look at NOR and NAND:

 

- Theorem: Any Boolean function that can be expressed as a truth table can be expressed using NAND and NOR.


- Proof sketch:

  

- How would you show that either NAND or NOR is sufficient?




# Relationship Among Representations

 

- \* Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.
 
# CL Block Example – 4 Bit Adder - where decomposition helps



$R = A + B$ ,  
c is carry out

- Truth Table Representation:

a3	a2	a1	a0	b3	b2	b1	b0	r3	r2	r1	r0	c
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	0	1	1	0	0	1	1	0
0	0	0	0	0	1	0	0	0	1	0	0	0
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	0	0	0	1	1	0	1	0	1	0
0	0	0	1	1	1	1	1	0	0	0	0	1

256 rows!

*In general:  $2^n$  rows for  $n$  inputs.*

*Is there a more efficient (compact) way to specify this function?*

# 4-bit Adder Example

- Motivate the adder circuit design by hand addition:

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 c \ r_3 \ r_2 \ r_1 \ r_0
 \end{array}$$

- Add  $a_0$  and  $b_0$  as follows:

a	b	r	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

*carry to next stage*

$$\begin{aligned}
 r &= a \text{ XOR } b = a \oplus b \\
 c &= a \text{ AND } b = ab
 \end{aligned}$$

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 c \ r_3 \ r_2 \ r_1 \ r_0
 \end{array}$$

- Add  $a_1$  and  $b_1$  as follows:

$c_i$	a	b	r	$co$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\begin{aligned}
 r &= a \oplus b \oplus c_i \\
 co &= ab + ac_i + bc_i
 \end{aligned}$$

# 4-bit Adder Example

- In general:


$$r_i = a_i \oplus b_i \oplus c_{in}$$
 
$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in} = c_{in}(a_i + b_i) + a_i b_i$$



*“Full adder cell”*

- Now, the 4-bit adder:

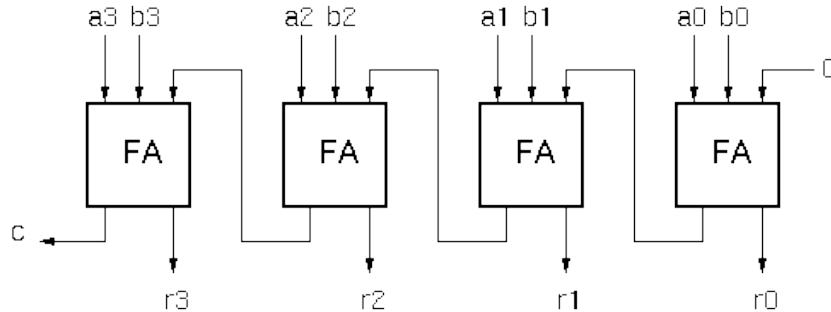


*“ripple” adder*

# Full-adder (FA) cell example
 
## □ Graphical Representation of FA-cell

$$r_i = a_i \oplus b_i \oplus c_{in}$$



$$c_{out} = a_i c_{in} + a_i b_i + b_i c_{in}$$




- Alternative Implementation (with only 2-input gates):

$$r_i = [a_i \oplus b_i] \oplus c_{in}$$
  
$$c_{out} = c_{in}[a_i + b_i] + a_i b_i$$



 

# Boolean Algebra

# Boolean Algebra

Set of elements  $B$ , binary operators  $\{+, \bullet\}$ , unary operation  $\{ '\}$ , such that the following axioms hold :

1.  $B$  contains at least two elements  $a, b$  such that  $a \neq b$ .

2. Closure :  $a, b$  in  $B$ ,

$$a + b \text{ in } B, a \bullet b \text{ in } B, a' \text{ in } B.$$

3. Communitive laws :

$$a + b = b + a, a \bullet b = b \bullet a.$$

4. Identities :  $0, 1$  in  $B$

$$a + 0 = a, a \bullet 1 = a.$$

5. Distributive laws :

$$a + (b \bullet c) = (a + b) \bullet (a + c), a \bullet (b + c) = a \bullet b + a \bullet c.$$

6. Complement :


$$a + a' = 1, a \bullet a' = 0.$$

$B = \{0,1\}$ ,  $+$  = OR,  $\bullet$  = AND,  $'$  = NOT


is a valid Boolean Algebra.



00		0
01		1
10		1
11		1

 

00		0
01		0
10		0
11		1

 

0		1
1		0

# Some Laws (theorems) of Boolean Algebra

Duality: A dual of a Boolean expression is derived by interchanging OR and AND operations, and interchanging 0s and 1s (the variables are left unchanged).

$$\{F(x_1, x_2, \dots, x_n, 0, 1, +, \bullet)\}^D = \{F(x_1, x_2, \dots, x_n, 1, 0, \bullet, +)\}$$

Any law that is true for an expression is also true for its dual.

Operations with 0 and 1:

$$\begin{array}{ll} \mathbf{x + 0 = x} & \mathbf{x * 1 = x} \\ \mathbf{x + 1 = 1} & \mathbf{x * 0 = 0} \end{array}$$

Idempotent Law:

$$\mathbf{x + x = x} \quad \mathbf{x * x = x}$$

Involution Law:

$$\mathbf{(x')' = x}$$

Laws of Complementarity:

$$\mathbf{x + x' = 1} \quad \mathbf{x * x' = 0}$$

Commutative Law:

$$\mathbf{x + y = y + x} \quad \mathbf{x * y = y * x}$$



# Some Laws (theorems) of Boolean Algebra (cont.)

Associative Laws:

$$(x + y) + z = x + (y + z)$$

$$x y z = x (y z)$$

Distributive Laws:

$$x (y + z) = (x y) + (x z)$$

$$x +(y z) = (x + y)(x + z)$$

“Simplification” Theorems:

$$x y + x y' = x$$

$$x + x y = x$$

$$x + x' y = x + y$$

$$(x + y) (x + y') = x$$

$$x (x + y) = x$$

$$x(x' + y) = xy$$

DeMorgan's Law:

$$(x + y + z + \dots)' = x' y' z'$$

$$(x y z \dots)' = x' + y' + z'$$

Theorem for Multiplying and Factoring:

$$(x + y) (x' + z) = x z + x' y$$


Consensus Theorem:

$$x y + y z + x' z = (x + y) (y + z) (x' + z)$$

$$x y + x' z = (x + y) (x' + z)$$

# DeMorgan's Law


$$(x + y)' = x' y'$$

 

*Exhaustive  
Proof*

x	y	x'	y'	(x+y)'	x'y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(x y)' = x' + y'$$

 


*Exhaustive  
Proof*

x	y	x'	y'	(xy)'	x'+y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0
 
# Relationship Among Representations

- \* Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



*How do we convert from one to the other?*

# Canonical Forms

- Standard form for a Boolean expression - unique algebraic expression directly from a true table (TT) description.
- Two Types:
  - \* **Sum of Products (SOP)**
  - \* **Product of Sums (POS)**
- Sum of Products [disjunctive normal form, minterm expansion]. Example:

Minterms	a	b	c	f	f'
a'b'c'	0	0	0	0	1
a'b'c	0	0	1	0	1
a'bc'	0	1	0	0	1
a'bc	0	1	1	1	0
ab'c'	1	0	0	1	0
ab'c	1	0	1	1	0
abc'	1	1	0	1	0
abc	1	1	1	1	0

One product (and) term for each 1 in f:

$$f = a'bc + ab'c' + ab'c + abc' + abc$$

$$f' = a'b'c' + a'b'c + a'bc'$$

*(enumerate all the ways the function could evaluate to 1)*

*What is the cost?*

# Sum of Products (cont.)

Canonical Forms are usually not minimal:

Our Example:

$$\begin{aligned} f &= a'bc + ab'c' + ab'c + abc' + abc & [xy' + xy = x] \\ &= a'bc + ab' + ab & [xy' + xy = x] \\ &= a'bc + a & [x'y + x = y + x] \\ &= a + bc \end{aligned}$$

$$\begin{aligned} f' &= a'b'c' + a'b'c + a'bc' & [xy' + xy = x] \\ &= a'b' + a'bc' & [x(y + z) = xy + xz] \\ &= a' ( b' + bc' ) & [x + x'y = x + y] \\ &= a' ( b' + c' ) & [x(y + z) = xy + xz] \\ &= a'b' + a'c' \end{aligned}$$

# Canonical Forms

- Product of Sums (conjunctive normal form, maxterm expansion). Example:

maxterms	a	b	c	f	f'
$a+b+c$	0	0	0	0	1
$a+b+c'$	0	0	1	0	1
$a+b'+c$	0	1	0	0	1
$a+b'+c'$	0	1	1	1	0
$a'+b+c$	1	0	0	1	0
$a'+b+c'$	1	0	1	1	0
$a'+b'+c$	1	1	0	1	0
$a'+b'+c'$	1	1	1	1	0


One sum (**or**) term for each **0** in f:

$$f = (a+b+c) (a+b+c') (a+b'+c)$$

$$f' = (a+b'+c') (a'+b+c) (a'+b+c') \\ (a'+b'+c) (a+b+c')$$

(enumerate all the ways the function could evaluate to 0)

What is the cost?

 

# Boolean Simplification

# Algebraic Simplification Example

Ex: full adder (FA) carry out function (in canonical form):

$$C_{out} = a'bc + ab'c + abc' + abc$$

ci	a	b	r	co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Algebraic Simplification

$$\begin{aligned} \text{Cout} &= a'bc + ab'c + abc' + abc \\ &= a'bc + ab'c + abc' + abc + abc \\ &= a'bc + abc + ab'c + abc' + abc \\ &= (a' + a)bc + ab'c + abc' + abc \\ &= (1)bc + ab'c + abc' + abc \\ &= bc + ab'c + abc' + abc + abc \\ &= bc + ab'c + abc + abc' + abc \\ &= bc + a(b' + b)c + abc' + abc \\ &= bc + a(1)c + abc' + abc \\ &= bc + ac + ab(c' + c) \\ &= bc + ac + ab(1) \\ &= bc + ac + ab \end{aligned}$$

# *Outline for remaining CL Topics*

- ❑ K-map method of two-level logic simplification
- ❑ Multi-level Logic
- ❑ NAND/NOR networks
- ❑ EXOR revisited

# Algorithmic Two-level Logic Simplification

Key tool: The Uniting Theorem:

$$xy' + xy = x(y' + y) = x(1) = x$$

<i>ab</i>	<i>f</i>
00	0
01	0
10	1
11	1

$$f = ab' + ab = a(b'+b) = a$$

b values change within the on-set rows

a values don't change

b is eliminated, a remains

<i>ab</i>	<i>g</i>
00	1
01	0
10	1
11	0

$$g = a'b'+ab' = (a'+a)b' = b'$$


b values stay the same

a values changes


b' remains, a is eliminated
 
# Karnaugh Map Method

- K-map is an alternative method of representing the TT and to help visual the adjacencies.







*Note: "gray code" labeling.*

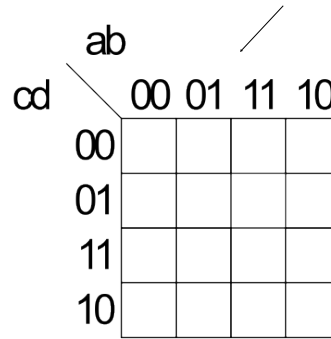

5 & 6 variable k-maps possible
    
# Karnaugh Map Method

- Adjacent groups of 1's represent product terms



# K-map Simplification

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
  - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
  - ✓ Form as large as possible groups and as few groups as possible.
  - ✓ Groups can overlap (this helps make larger groups)
  - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
  - the term includes the “constant” variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

# K-maps (cont.)

		ab			
		00	01	11	10
c	0	1	0	0	1
	1	0	0	1	1

$$f = b'c' + ac$$

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = c + a'bd + b'd'$$

(bigger groups are better)

# Product-of-Sums K-map

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
  - the term includes the “constant” variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1


$$f = (b' + c + d)(a' + c + d')(b + c + d')$$



# BCD incrementer example

## Binary Coded Decimal

	<i>a b c d</i>	<i>w x y z</i>
0	0000	0001
1	0001	0010
2	0010	0011
3	0011	0100
4	0100	0101
5	0101	0110
6	0110	0111
7	0111	1000
8	1000	1001
9	1001	0000
	1010	- - - -
	1011	- - - -
	1100	- - - -
	1101	- - - -
	1110	- - - -
	1111	- - - -

 

# BCD Incrementer Example

- ❑ Note one map for each output variable.
- ❑ Function includes “don’t cares” (shown as “-” in the table).
  - These correspond to places in the function where we don’t care about its value, because we don’t expect some particular input patterns.
  - We are free to assign either 0 or 1 to each don’t care in the function, as a means to increase group sizes.
- ❑ In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.

# BCD incrementer example

**W**

		ab			
cd		00	01	11	10
00	0	0	-	1	
01	0	0	-	0	
11	0	1	-	-	
10	0	0	-	-	

**X**

		ab			
cd		00	01	11	10
00	0	1	-	0	
01	0	1	-	0	
11	1	0	-	-	
10	0	1	-	-	

w =

x =

**y**

		ab			
cd		00	01	11	10
00	0	0	-	0	
01	1	1	-	0	
11	0	0	-	-	
10	1	1	-	-	



**z**


		ab			
cd		00	01	11	10
00	1	1	-	1	
01	0	0	-	0	
11	0	0	-	-	
10	1	1	-	-	

y =

z =

# Higher Dimensional K-maps

 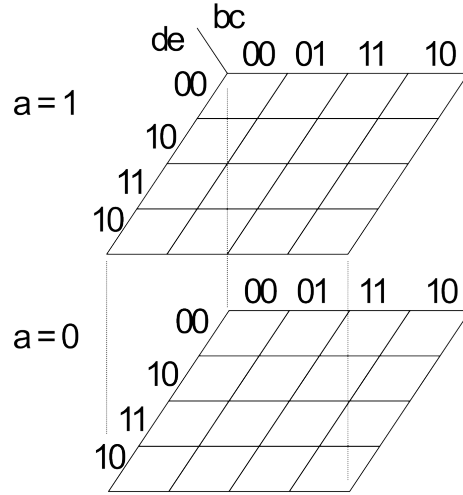

 

## Boolean Simplification – Multi-level Logic

# Multi-level Combinational Logic



- Example: reduced sum-of-products form
$$x = adf + aef + bdf + bef + cdf + cef + g$$
- Implementation in 2-levels with gates:
  - cost:** 1 7-input OR, 6 3-input AND
  - $\Rightarrow$  ~50 transistors
  - delay:** 3-input OR gate delay + 7-input AND gate delay

- Factored form:

$$x = (a + b + c)(d + e)f + g$$

**cost:** 1 3-input OR, 2 2-input OR, 1 3-input AND  
 $\Rightarrow$  ~20 transistors

  **delay:** 3-input OR + 3-input AND + 2-input OR




*Footnote: NAND would be used in place of all ANDs and ORs.*

## Which is faster?


*In general: Using multiple levels (more than 2) will reduce the cost. Sometimes also delay. Sometimes a tradeoff between cost and delay.*
 
# Multi-level Combinational Logic

Another Example:  $F = abc + abd + a'c'd' + b'c'd'$



let  $x = ab$   $y = c+d$

 

$f = xy + x'y'$

Incorporates fanout.

No convenient hand methods exist for multi-level logic simplification:

a) CAD Tools use sophisticated algorithms and heuristics

Guess what? These problems tend to be NP-complete

b) Humans and tools often exploit some special structure (example adder)

# NAND-NAND & NOR-NOR Networks





DeMorgan's Law Review:

$$(a + b)' = a' b'$$

$$a + b = (a' b')'$$

$$(a b)' = a' + b'$$

$$a b = (a' + b')'$$

    


*push bubbles or introduce in pairs or remove pairs:*  $(x')' = x$



# NAND-NAND & NOR-NOR Networks


□ Mapping from AND/OR to NAND/NAND

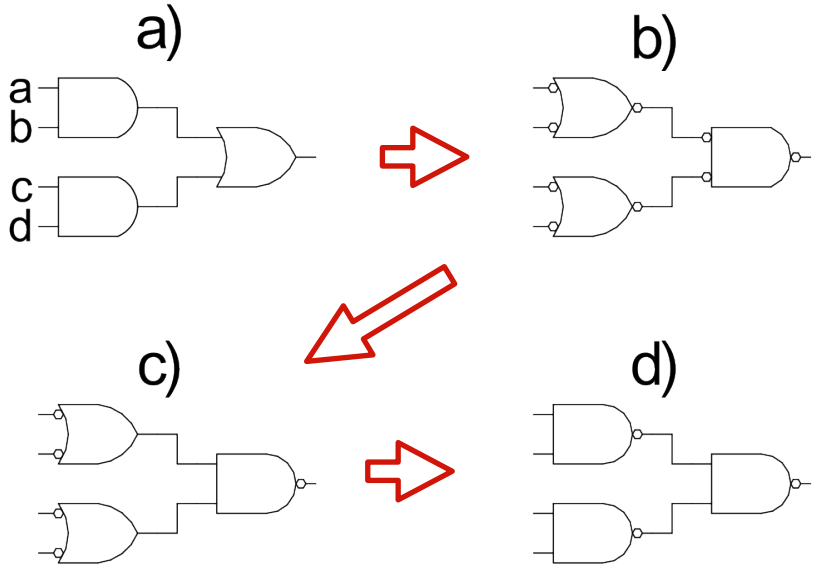

# Multi-level Networks

Convert to NANDs:

$$F = a(b + cd) + bc'$$

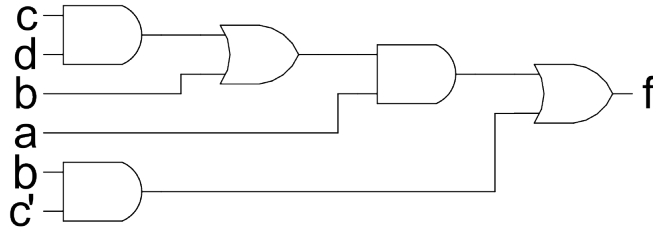


# EXOR Function Implementations

Parity, addition mod 2

$$x \oplus y = x'y + xy'$$

x	y	xor	xnor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 

Another approach:

